

# PDS0101

Introduction to Digital Systems

Boolean Algebra and Logic Simplification

# Lecture outcome


- ✂ By the end of today's lecture you should know
  - the basic rules on boolean algebra
  - DeMorgan's theorems
  - how to perform simplification of logic circuit diagrams and boolean expressions using the above

# Boolean algebra


- ∞ Boolean algebra is the mathematics of digital systems.
- ∞ A basic knowledge of boolean algebra is indispensable to the study and analysis of logic circuits.
- ∞ *Variable, complement* and *literal* are terms used in boolean algebra.
- ∞ A literal is a variable or its complement
  - A variable is a symbol used to represent logical quantity.
    - Any single variable can have a 1 or a 0 value.
  - The complement represents the inverse of a variable and is indicated with an overbar. Thus, the complement of A is  $\bar{A}$ .
  - To simplify entry, some use the apostrophe to indicate complement  
→ the complement of B is B'
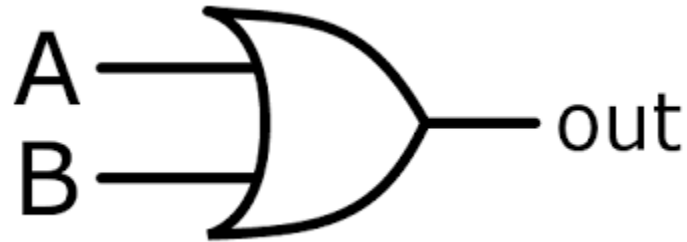
# Boolean addition and multiplication

- Boolean addition is equivalent to OR operation



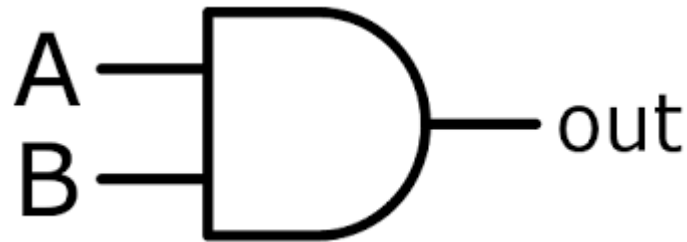- Boolean multiplication is equivalent to AND operation




# Boolean algebra rules

- ✎ In algebra, we learned rules or laws
- ✎ For example the *commutative law of addition*
$$A + B = B + A$$
  - where A and B are any whole number (in 6th grade) or A and B are any real number (in 9th grade)
- ✎ In 1860 George Boole developed an algebra where A and B were only allowed to be true or false → this is called *Boolean algebra* and is used in digital electronics.
- ✎ Boolean algebra laws and rules are similar to the algebra, but only 1 or 0 is allowed for the values in variables
- ✎ The following slides show basic rules of boolean algebra
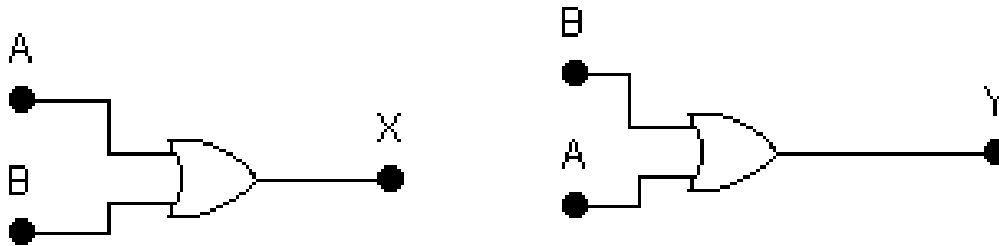
# Commutative law of addition


- ∞  $A+B = B+A$
- ∞ The order of OR-ing does not matter



$$X = Y$$
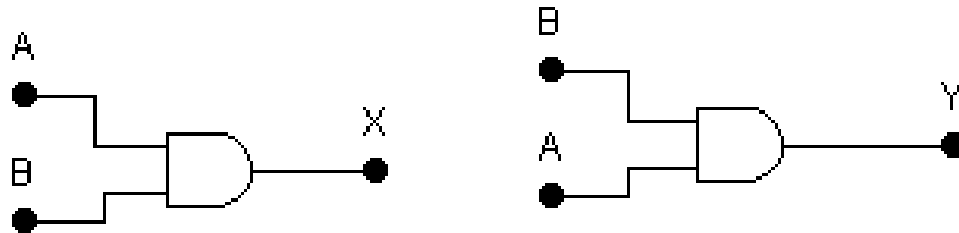
# Commutative law of multiplication

- ∞  $AB = BA$
- ∞ The order of ANDing does not matter.





$$X = Y$$
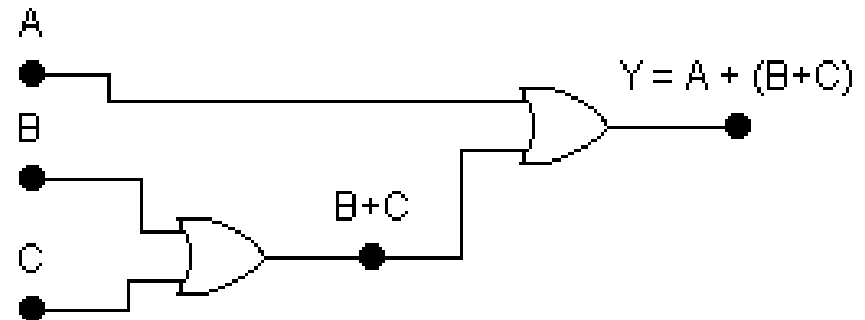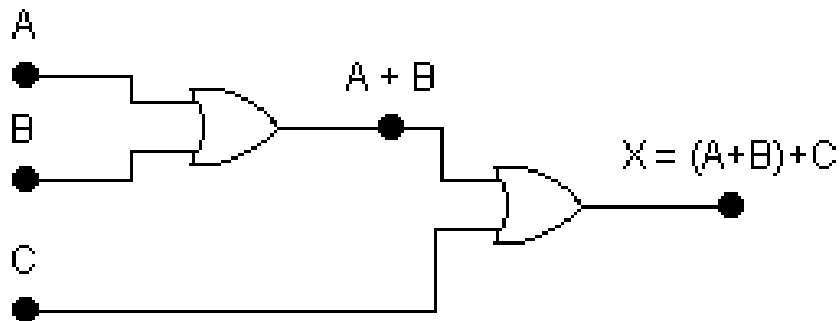
# Associative law of addition

∞  $A + (B + C) = (A + B) + C$

∞ The grouping of ORed variables does not matter





$$X = Y$$


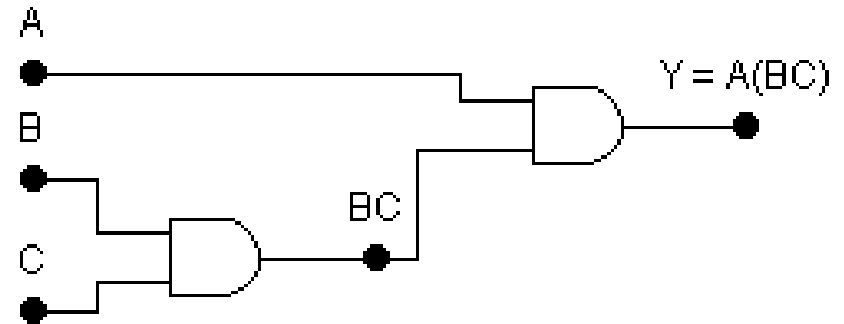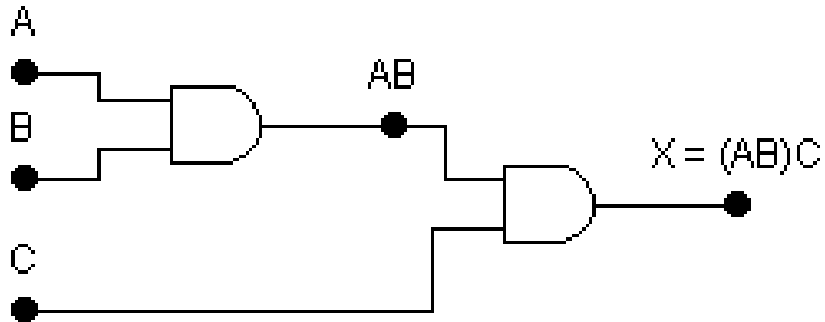
# Associative law of multiplication

∞  $A(BC) = (AB)C$


∞ The grouping of ANDed variables does not matter





$$X = Y$$
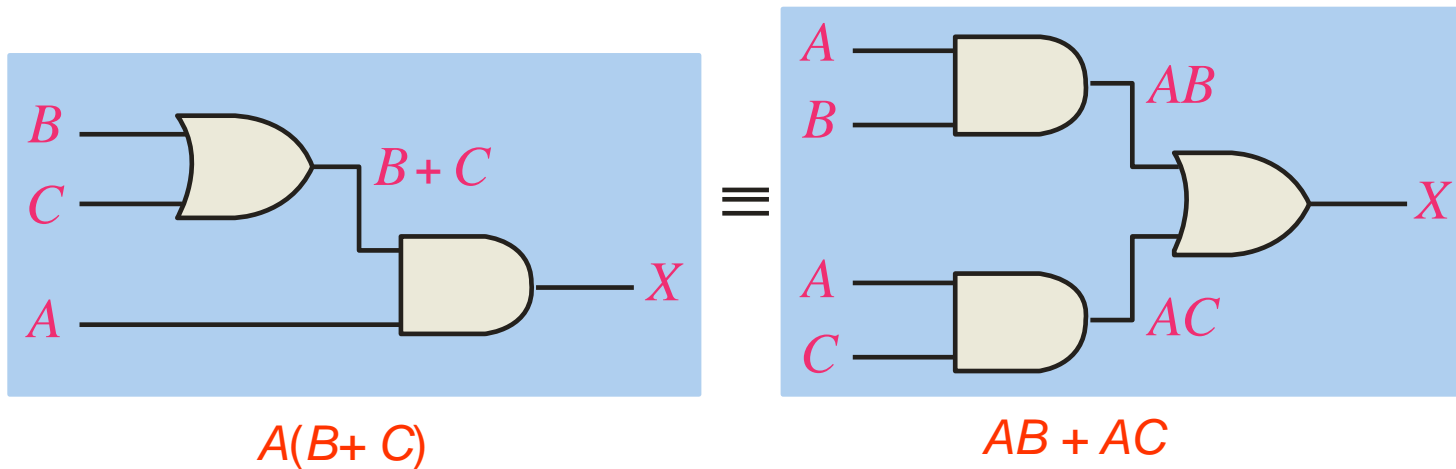
# Distributive Law 1

- ∞ The distributive law is the factoring law. A common variable can be factored from an expression just as in ordinary algebra
- ∞  $A(B + C) = AB + AC$




# Proof

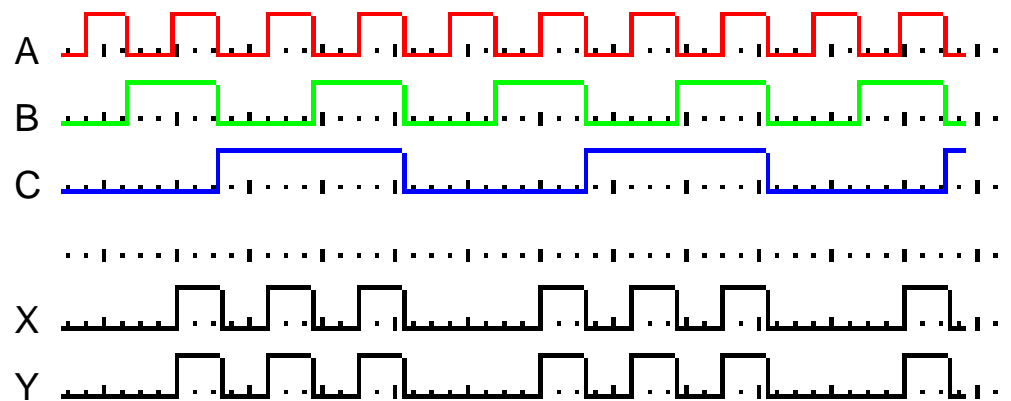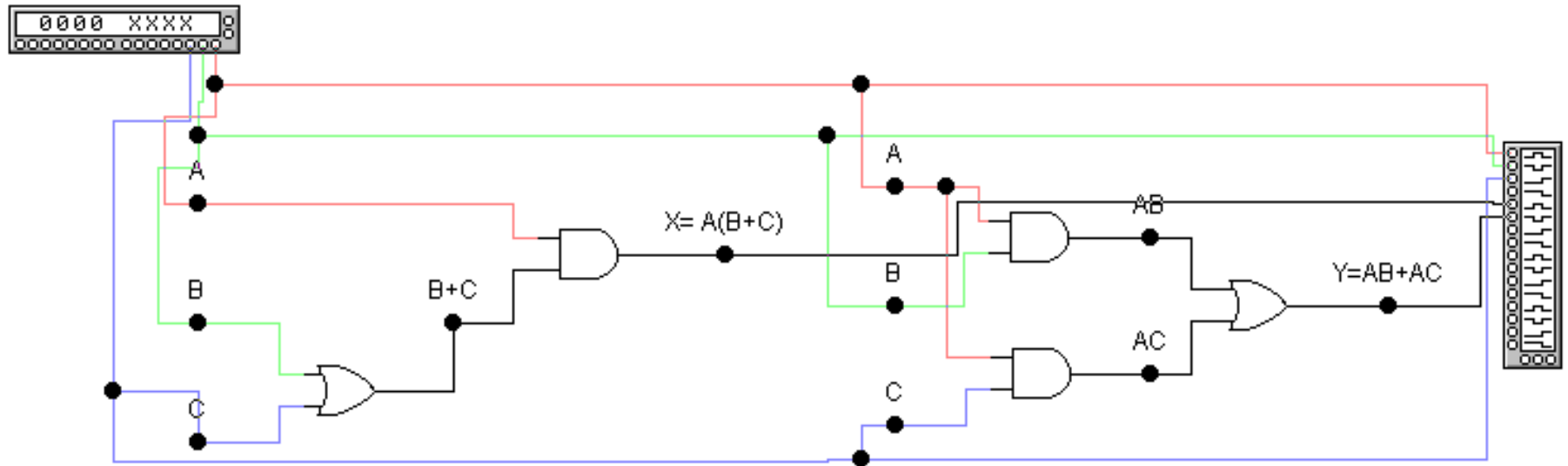



# Distributive Law 2

∞  $(A+B)(C+D) = AC + AD + BC + BD$

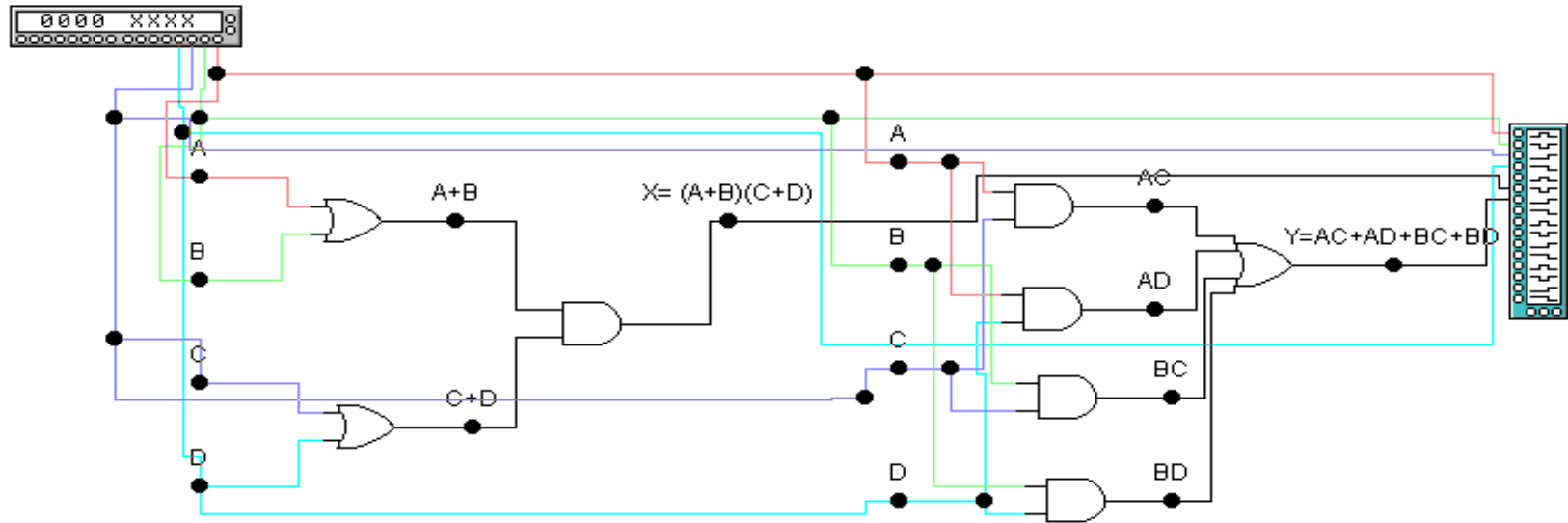



$$X = Y$$

# Proof

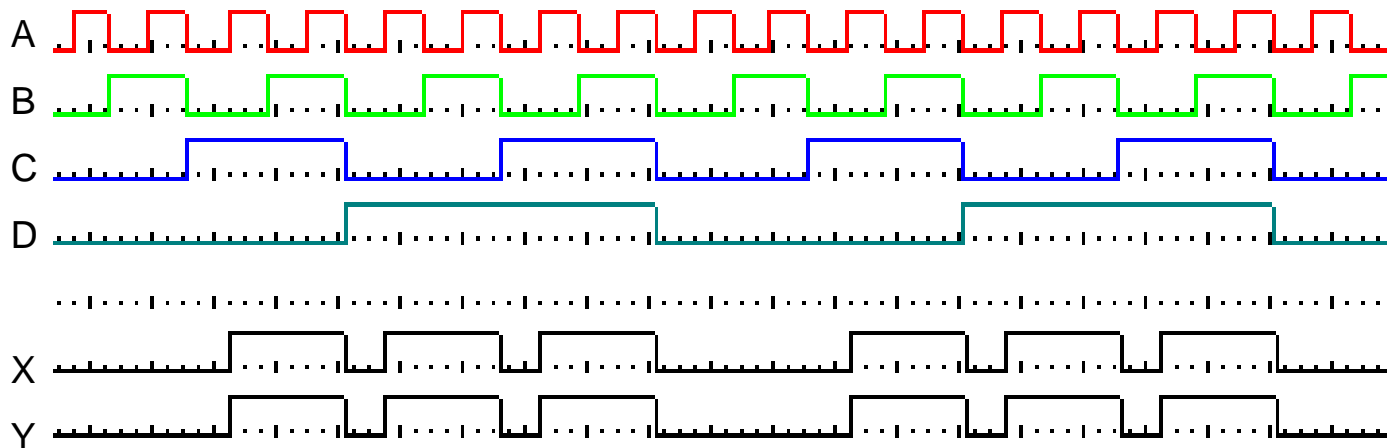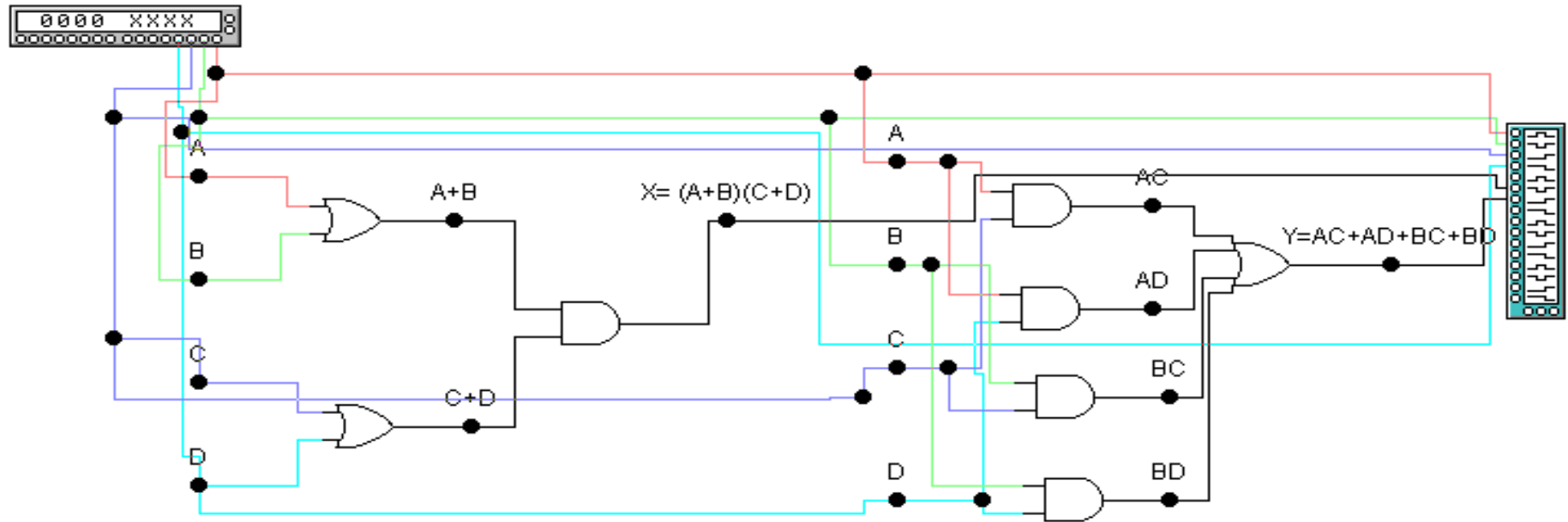

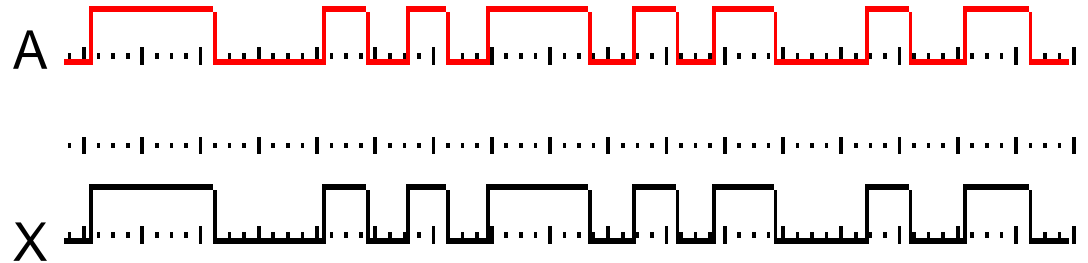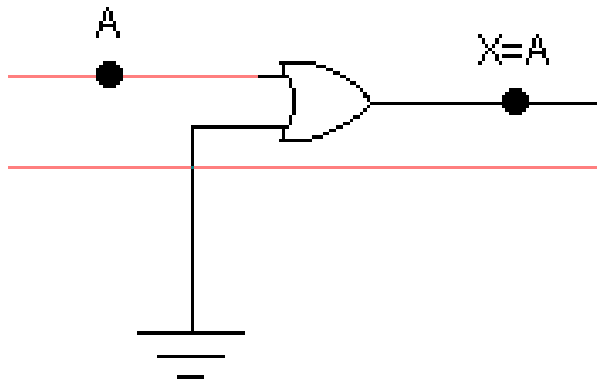
# $A+0=A$

- ∞ In math if you add 0 you have changed nothing
- ∞ In Boolean Algebra ORing with 0 changes nothing



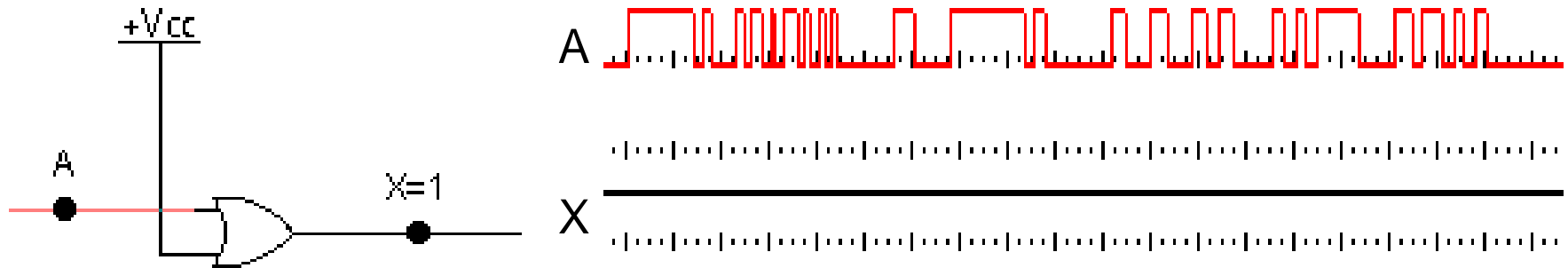
# $A+1=1$

- OR-ing with 1 must give a 1 since if any input is 1 to an OR gate will give a 1


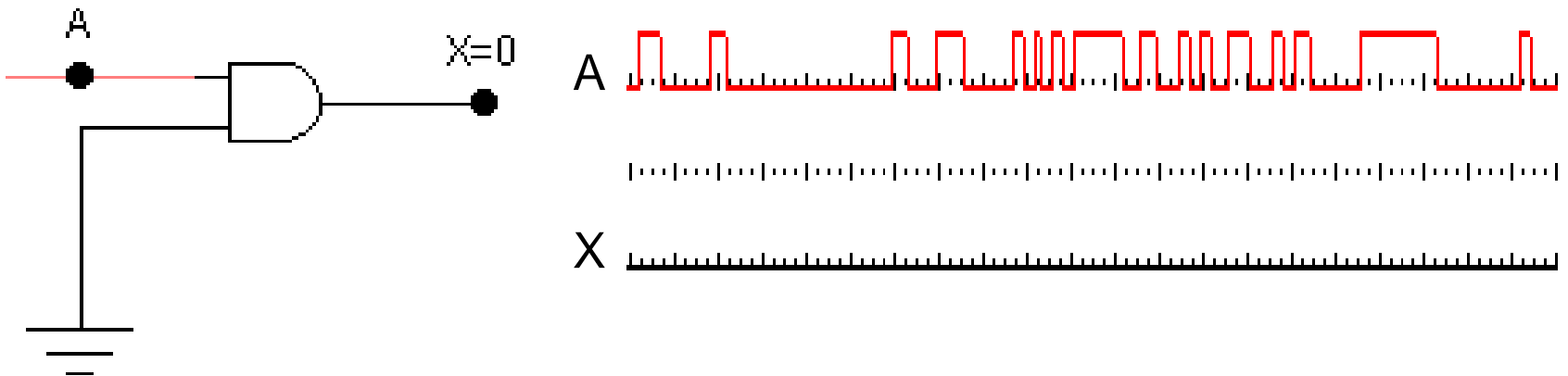
# $A \cdot 0 = 0$


- ∞ In math if 0 is multiplied with anything you get 0.
- ∞ So if you AND anything with 0 you get 0






$$A \cdot 1 = A$$

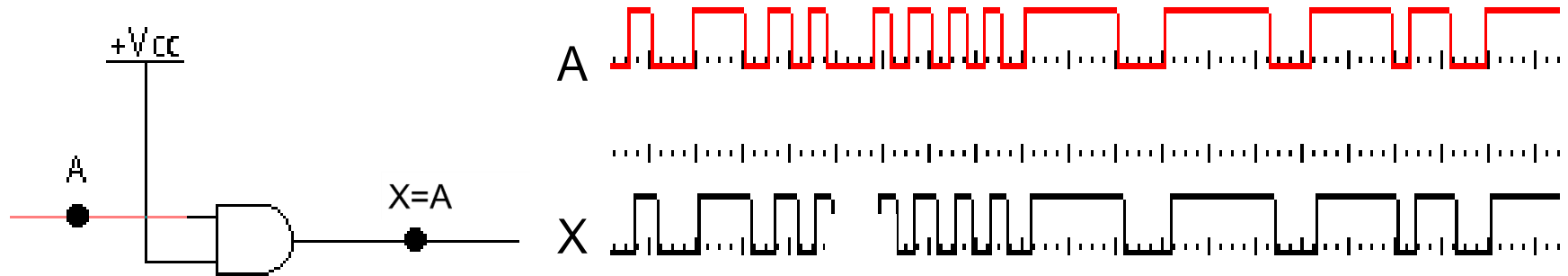∞ ANDing anything with 1 will yield back anything





$$A + A = A$$

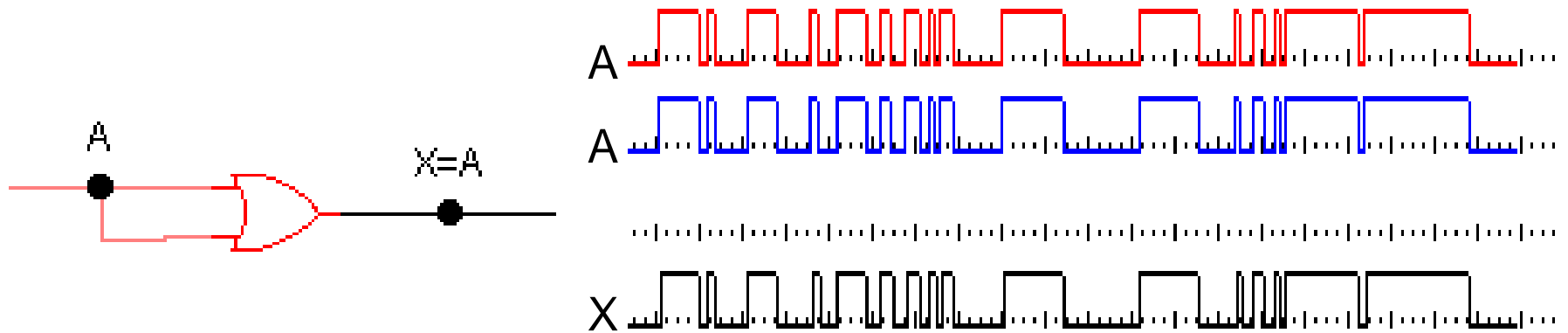∞ ORing with itself will give the same result





$$A + \bar{A} = 1$$

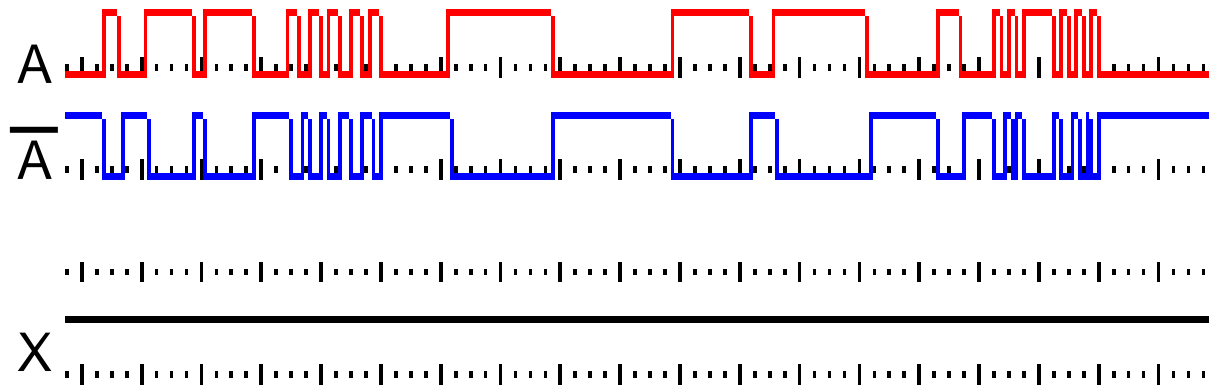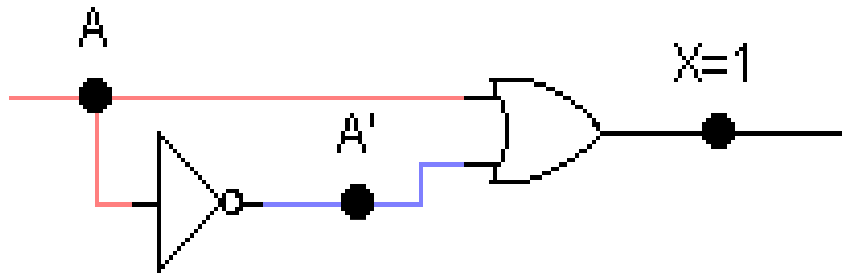∞ Either A or  $\bar{A}$  must be 1 so  $A + \bar{A} = 1$





$$A \cdot A = A$$

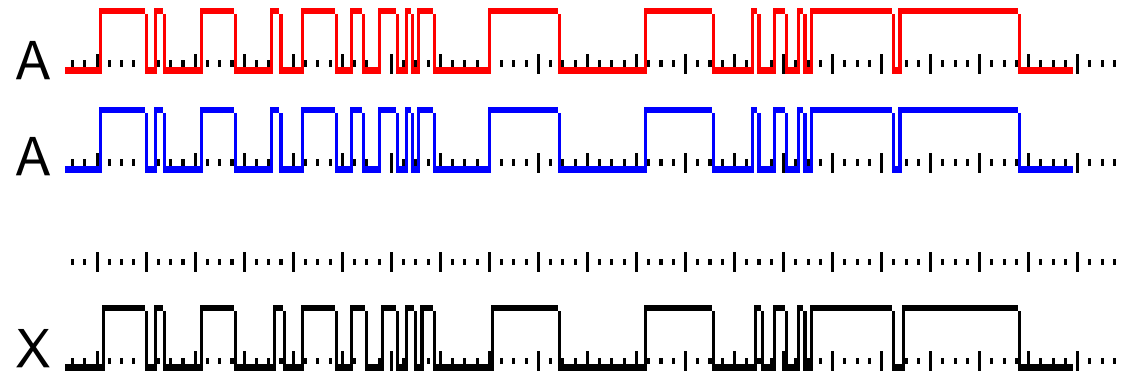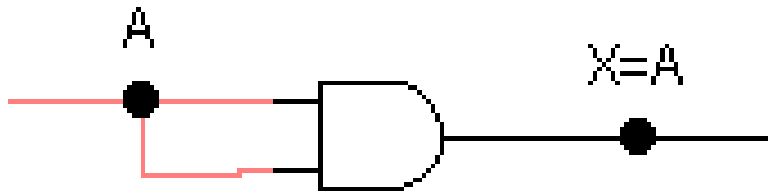∞ AND-ing with itself will give the same result





$$A \cdot \bar{A} = 0$$

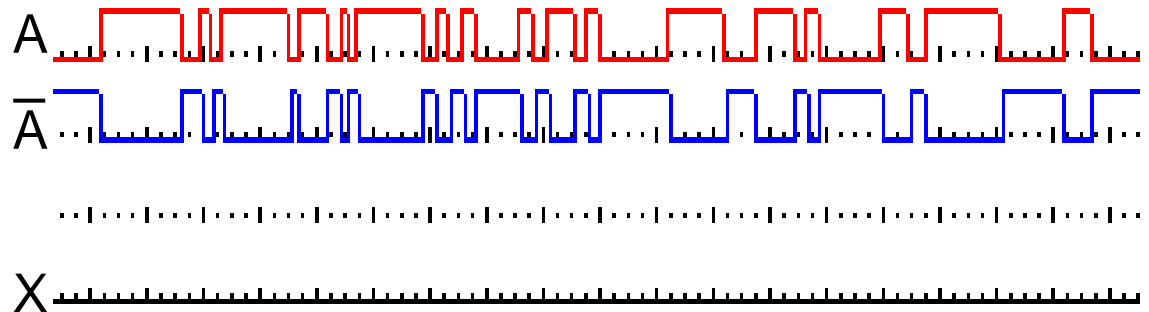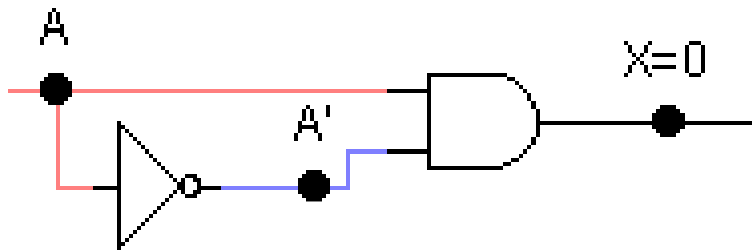- ∞ In digital logic if  $A = 1$  then  $A' = 0$ , i.e. either  $A$  or  $A' = 0$ , so  $AA' = 0$  since one of the inputs must be 0.





$$\overline{\overline{A}} = A$$

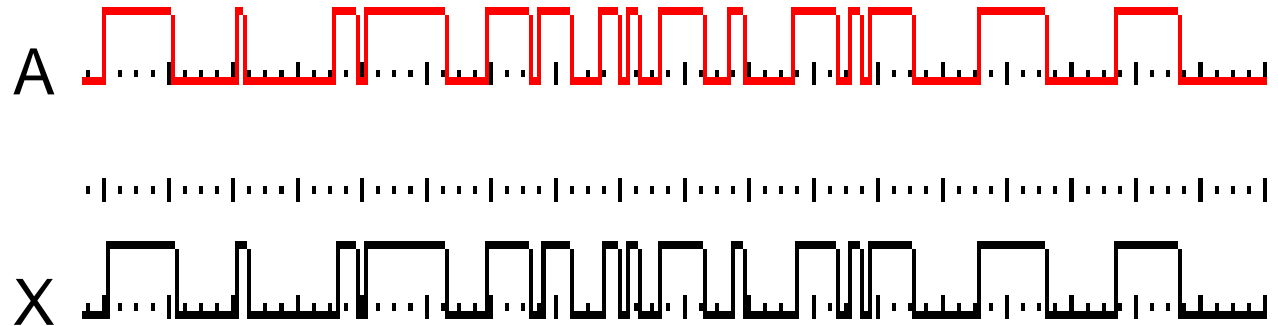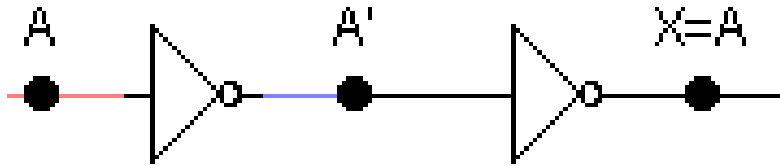∞ If you invert any input twice you are back to the beginning



# $A + AB = A$

∞  $A + AB = A(1 + B) = A(1) = A$

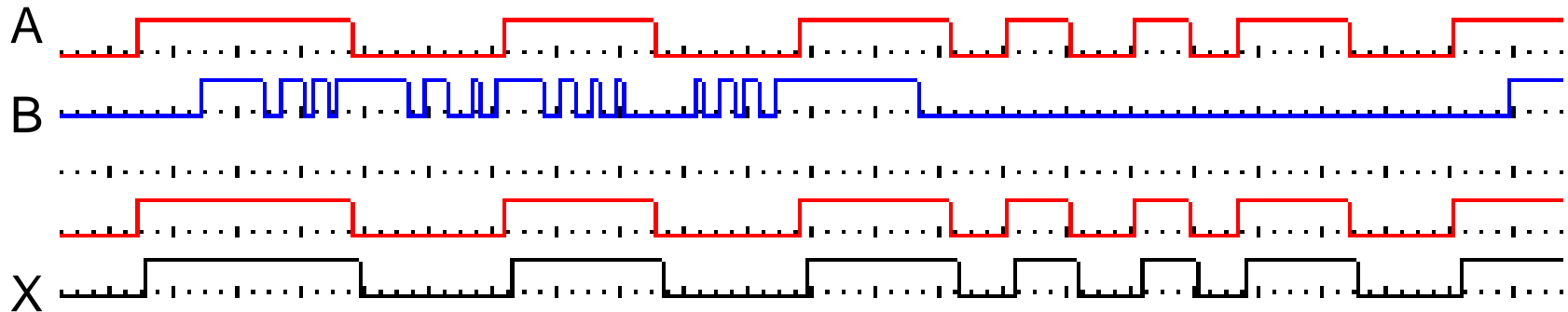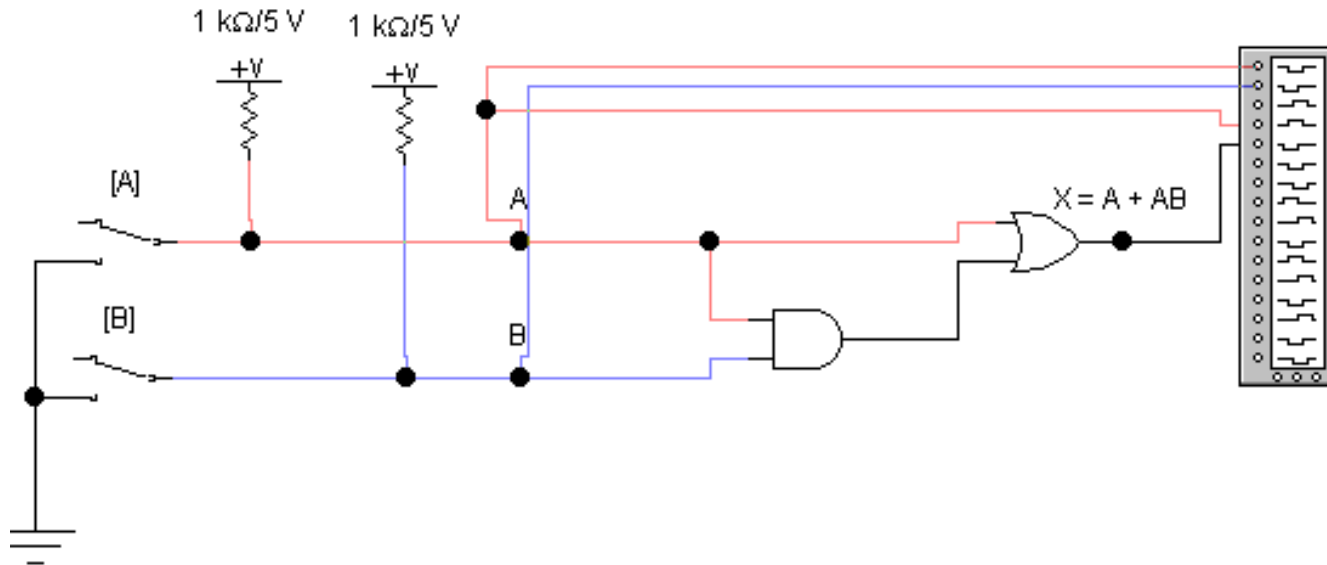

$$A + \overline{A}B = A + B$$

∞ If A is 1 the output is 1, If A is 0 the output is B



$$\begin{aligned} A + \overline{A}B &= (A + AB) + \overline{A}B && \leftarrow \text{rule 10} \\ &= (AA + AB) + \overline{A}B && \leftarrow \text{rule 7} \\ &= AA + AB + A\overline{A} + \overline{A}B && \leftarrow \text{rule 8} \\ &= (A + \overline{A})(A + B) && \leftarrow \text{rule 12} \\ &= 1 \cdot (A + B) = A + B && \leftarrow \text{rule 4} \end{aligned}$$

∞ What about  $A' + AB$ ?

$$\begin{aligned} A' + AB &= A'(B + B') + AB \\ &= A'B + A'B' + AB \\ &= (A' + A)B + A'B' \\ &= B + A'B' \\ &= A' + B \end{aligned}$$



# Proof

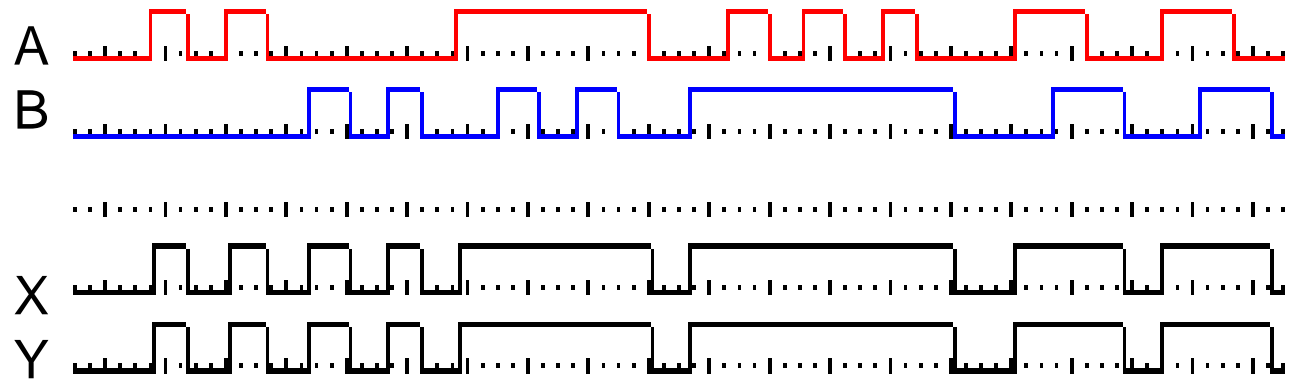
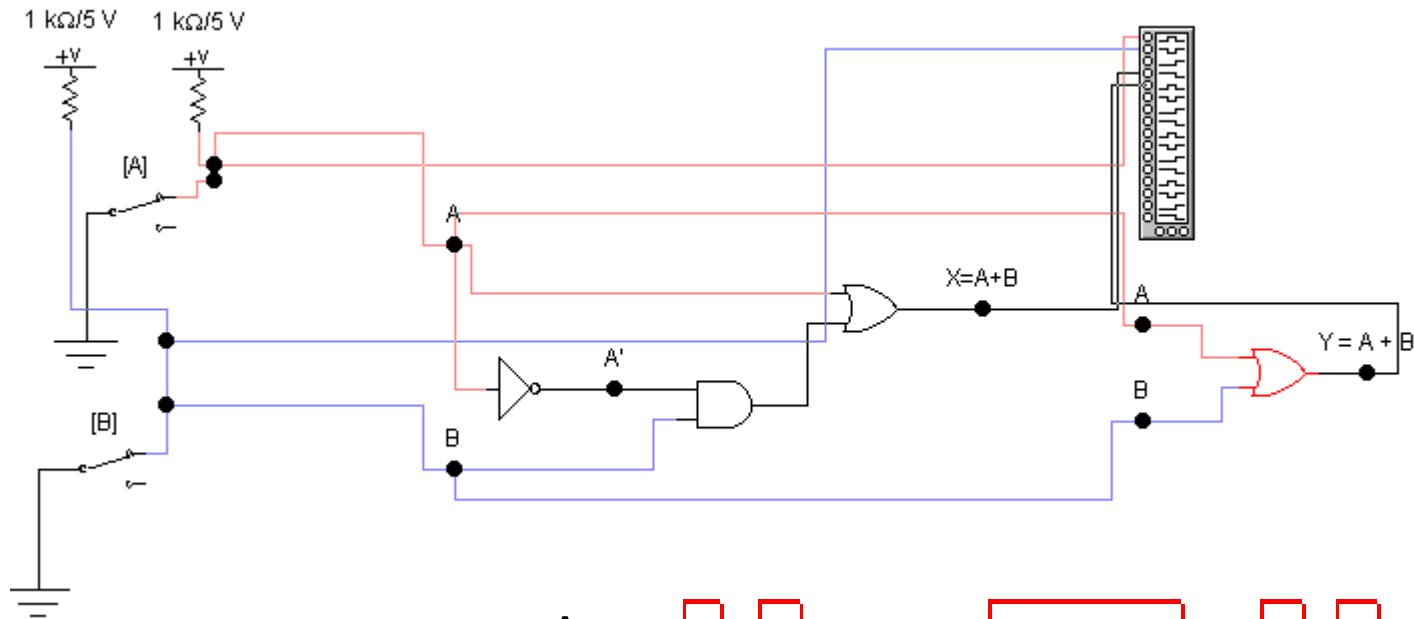


$$(A + B)(A + C) = A + BC$$

∞  $(A + B)(A + C)$

$$\begin{aligned} &= AA + AC + BA + BC \\ &= A + AC + BA + BC \\ &= A(1 + C + B) + BC \\ &= A + BC \end{aligned}$$

# Proof

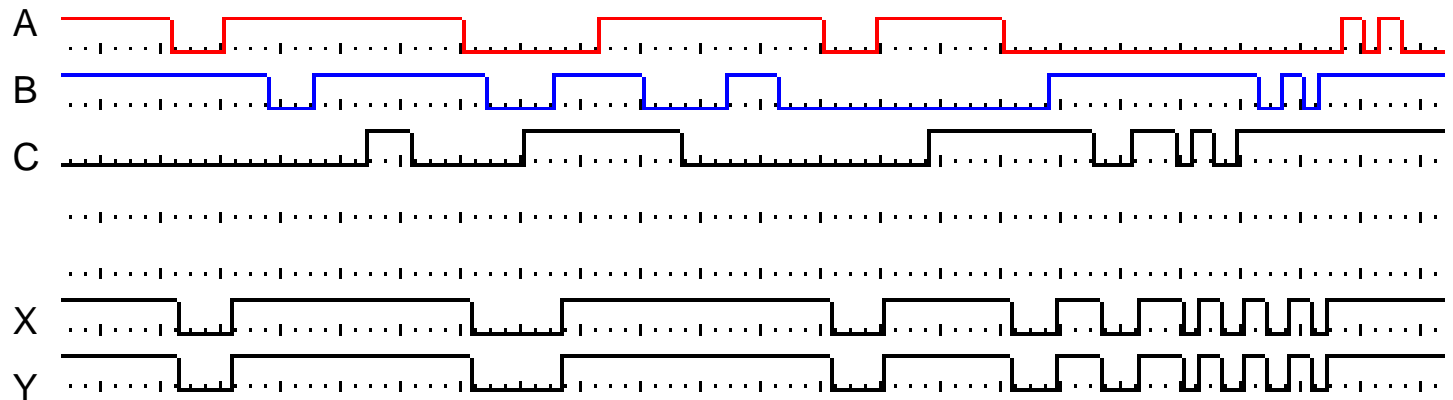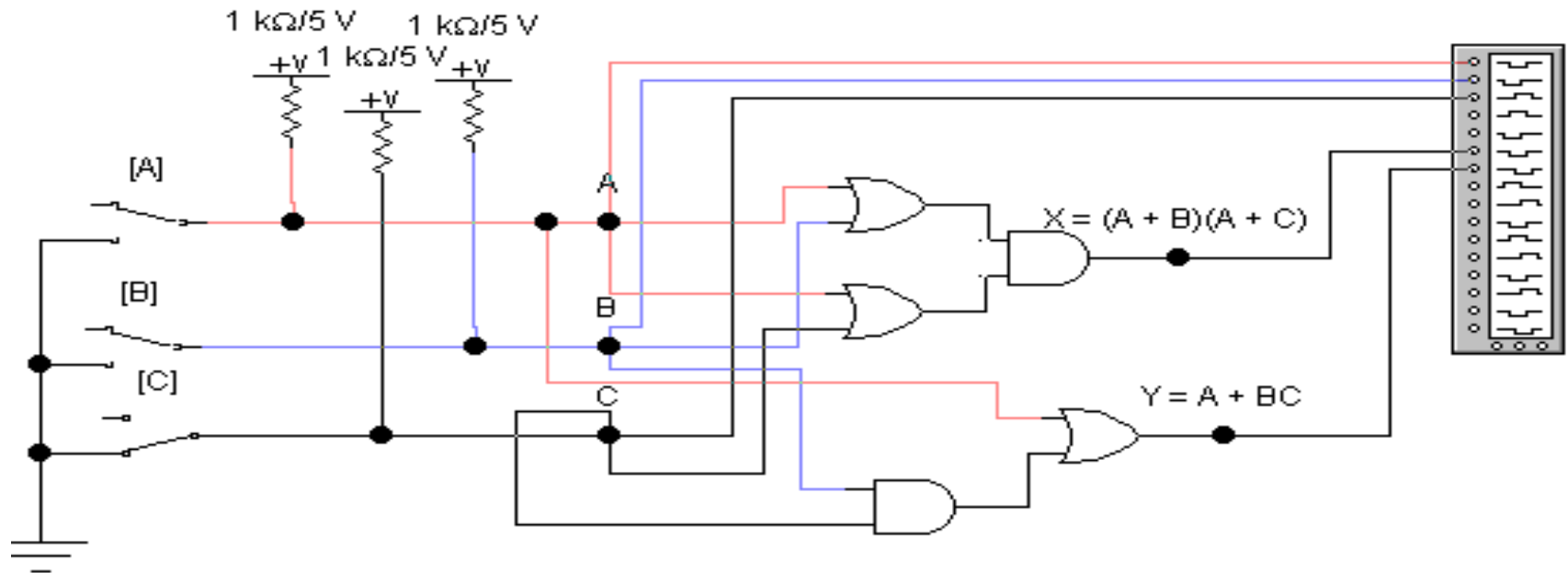

# DeMorgan's Theorem

- ∞ DeMorgan's theorems provide mathematical verification of the equivalency of the NAND gate and negative-OR gates and equivalency of the NOR and negative- AND gates.
- ∞ These theorems are extremely useful in simplifying expressions in which a product or sum of variables is inverted
  - DeMorgan will help to simplify digital circuits using NORs and ANDs his theorem states


# DeMorgan's Theorem

- De Morgan's first theorem:

*The complement of a product of variables is equal to the sum of the complements of the variables.*

- Stated another way,
- The complement of two or more variables ANDed is equivalent to the OR of the complements of the individual variables.
- The formula for expressing this theorem for two variables is:
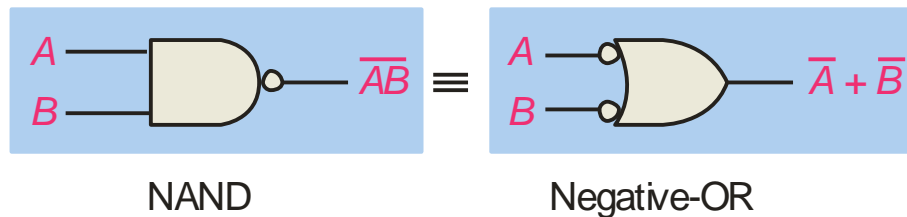
$$\overline{AB} = \overline{A} + \overline{B}$$



Inputs		Output	
A	B	$\overline{AB}$	$\overline{A} + \overline{B}$
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

# DeMorgan's Theorem

## Second theorem:


*The complement of a sum of variables is equal to the product of the complements of the variables.*

Stated in another way,

The complement of two or more variables ORed is equivalent to the AND of the complements of the individual variables

The formula for expressing this theorem:
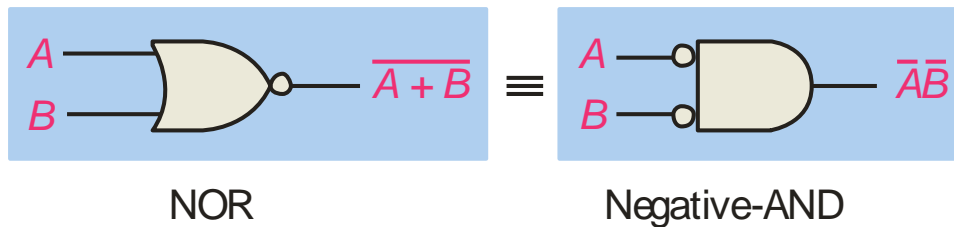
$$\overline{A + B} = \overline{A} \cdot \overline{B}$$



Inputs		Output	
A	B	$\overline{A + B}$	$\overline{A} \overline{B}$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

# Rules and theorems of Boolean algebra

1.  $A+0 = A$

2.  $A+1 = 1$

3.  $A.0 = 0$

4.  $A.1 = A$

5.  $A+A = A$

6.  $A+A'=1$       ( $\overline{A} + A = 1$ )

7.  $A.A = A$

8.  $A'.A = 0$       ( $\overline{A}.A = 0$ )

9.  $A'' = A$       ( $\overline{\overline{A}} = A$ )

10.  $A+AB = A$

11.  $A+A'B = A+B$       ( $A + \overline{A}B = A+B$ )

12.  $(A+B)(A+C) = A+BC$

13.  $(AB)' = A' + B'$       ( $\overline{AB} = \overline{A} + \overline{B}$ )

14.  $(A + B)' = A'B'$       ( $\overline{A+B} = \overline{A}.\overline{B}$ )

# Boolean Analysis of Logic Circuits


- ∞ The purpose of this section is to practice changing gates to simplified Boolean Algebra expressions.
- ∞ Combinational logic circuits can be analyzed by writing the expression for each gate and combining the expressions according to the rules for Boolean algebra
  - Simplification of the Boolean is also done using the Boolean Laws and rules.



# Examples
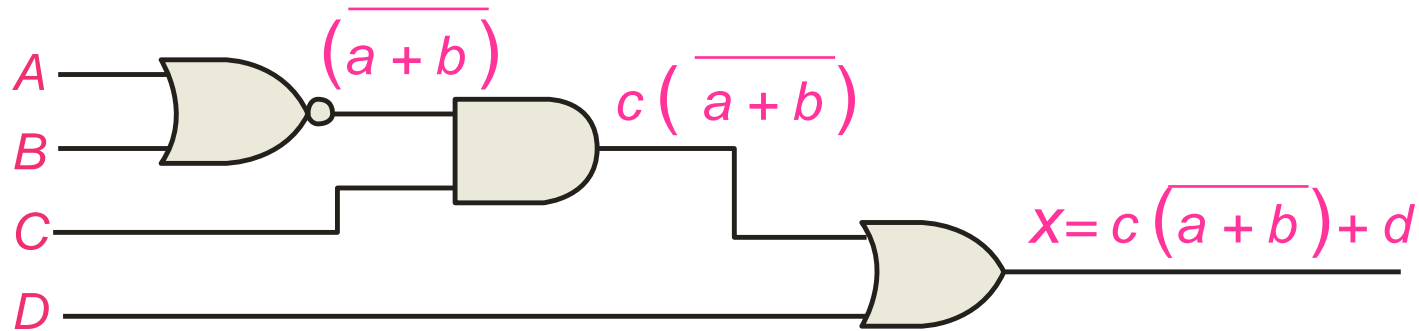
## Example 1

Apply Boolean algebra to derive the expression for X.




## Solution


Write the expression for each gate

$$X = \overline{C(A+B)} + D$$

## Example 2

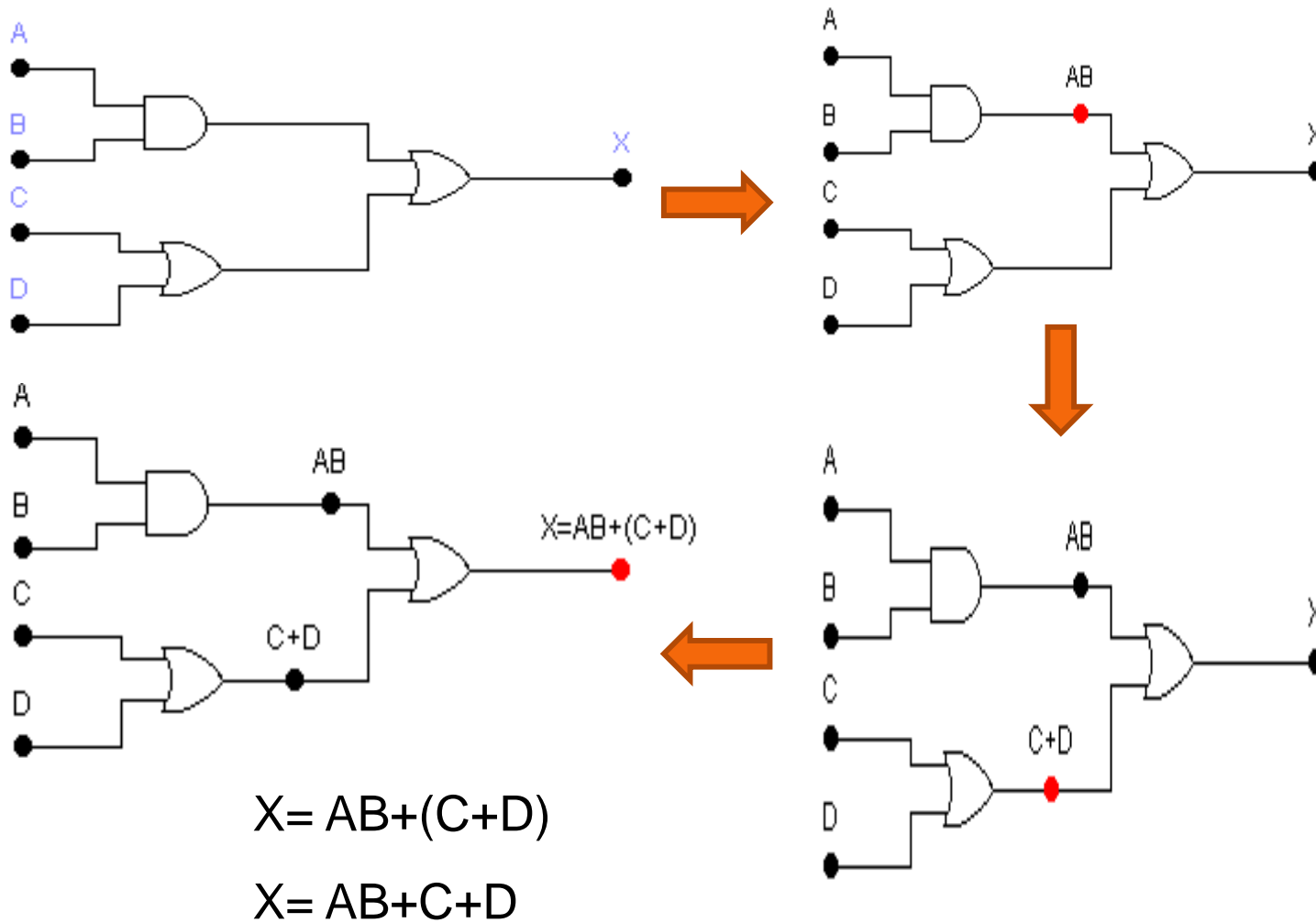


### Example 3

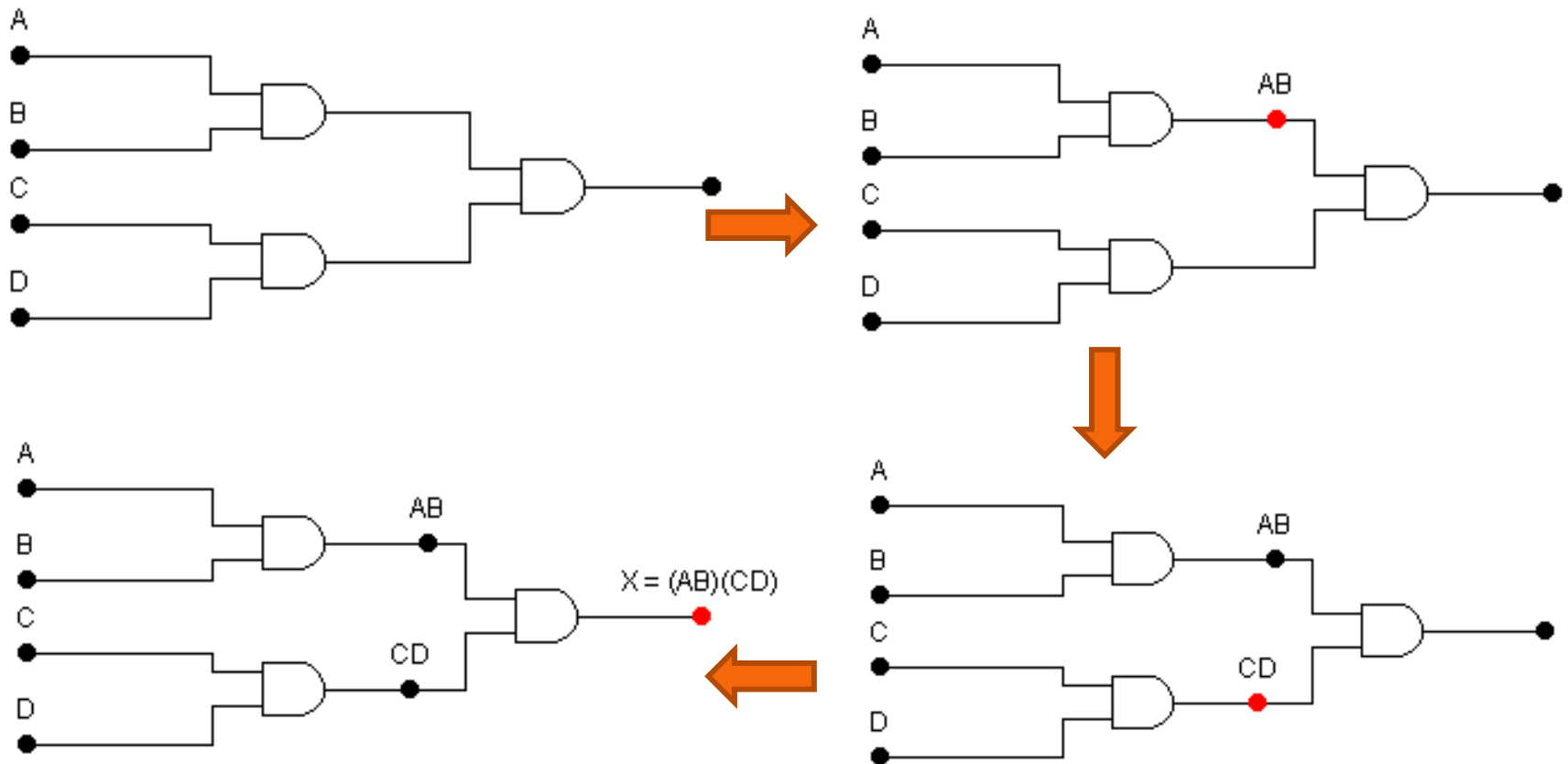

$$X = (AB)(CD)$$

$$X = ABCD$$

## Example 4

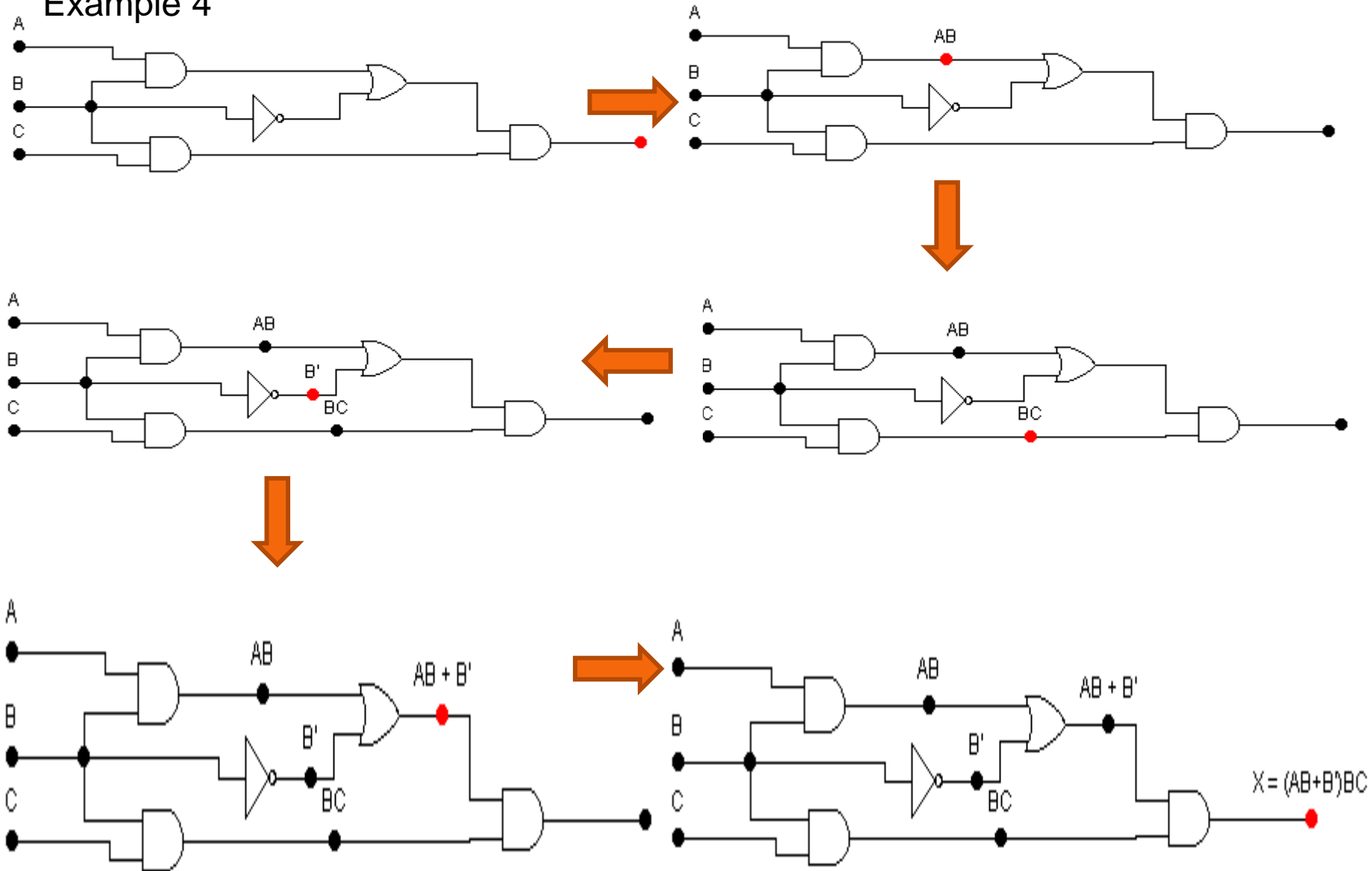

# Boolean logic simplification

- ∞ We will see the circuit from the slide before can be simplified with the following circuit and see they do the same thing

$$X = (AB + \overline{B})BC$$

using distributive law

$$X = A\textcolor{red}{B}B\textcolor{red}{C} + \overline{B}B\textcolor{red}{C}$$



$$X = ABC + \overline{B}\textcolor{red}{B}\textcolor{red}{C}$$

$$X = ABC + \textcolor{red}{0}\cdot\textcolor{red}{C}$$

$$X = ABC + 0$$

$$X = ABC$$

# Proof

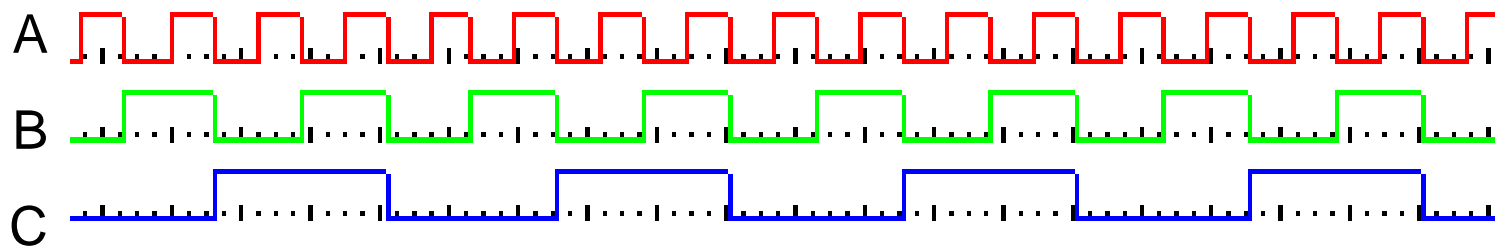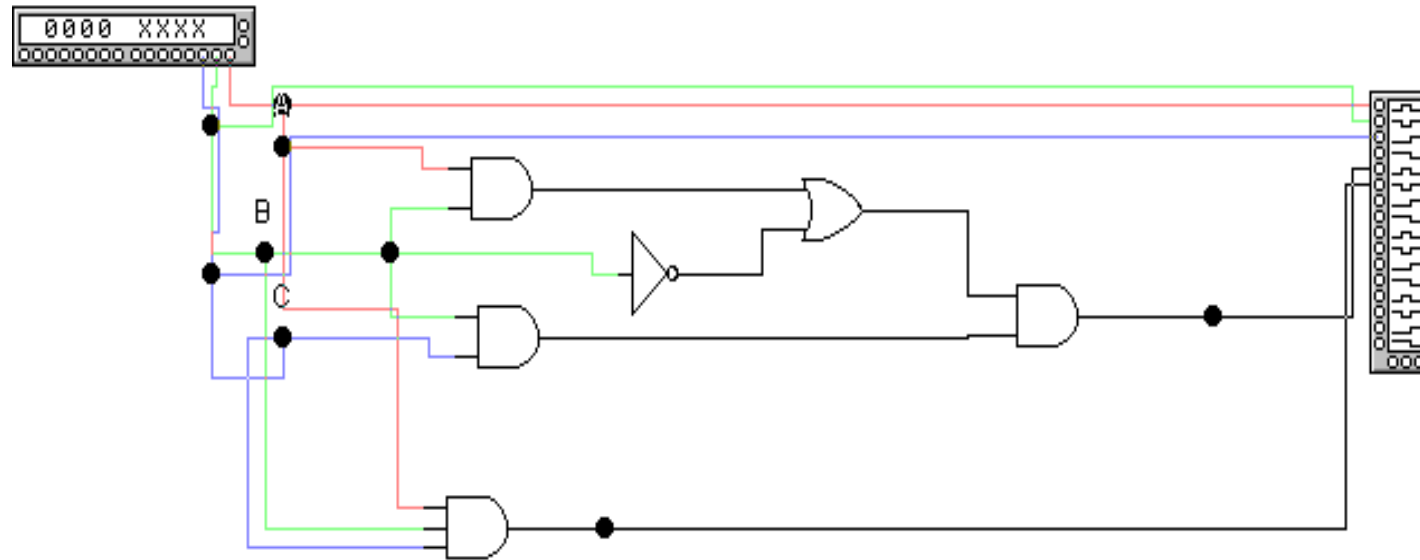


.....

$X = (AB + B)BC$  .....


$Y = ABC$  .....

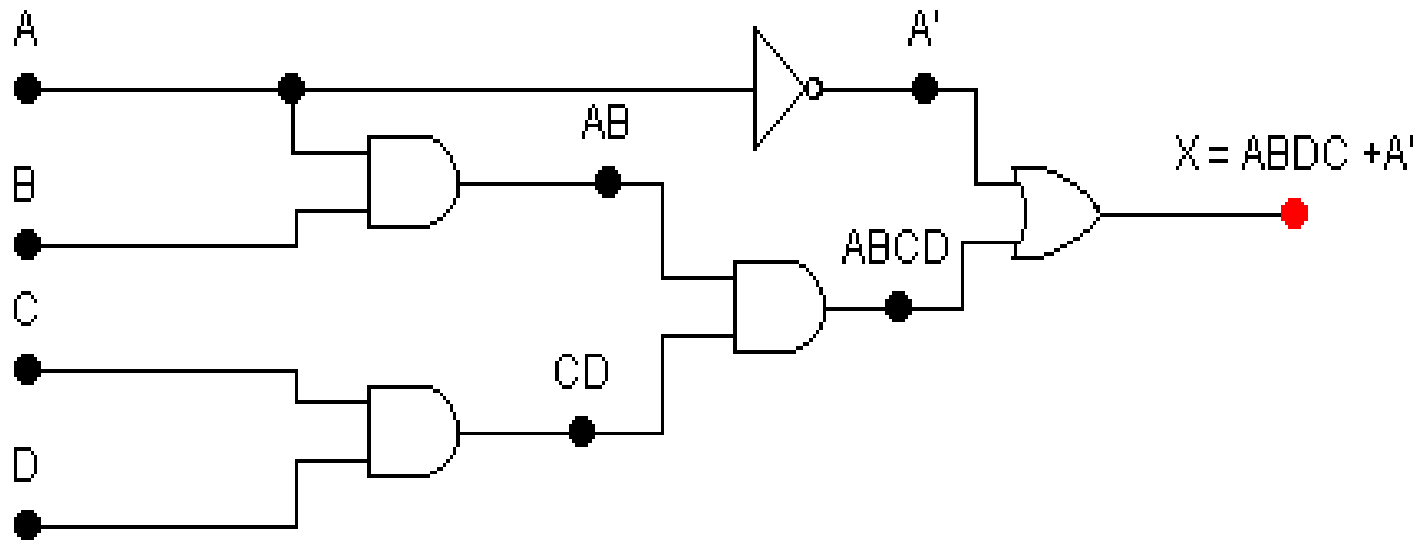Using example 3 from earlier slides, simplify the equation obtained




$$\begin{aligned} X &= ABCD + \overline{A} \\ &= \overline{A} + BCD \end{aligned}$$
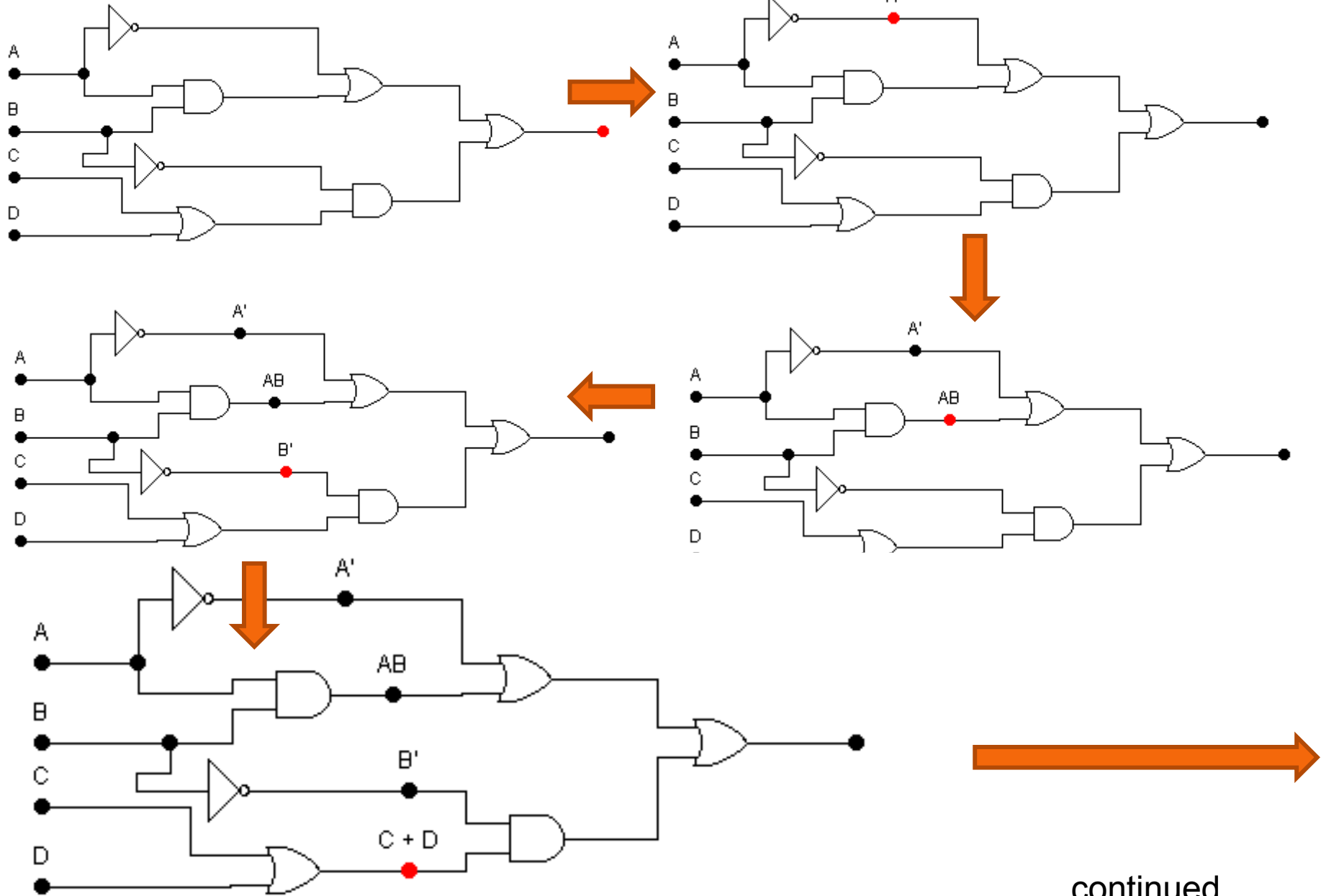
## Example 5 – Simplify the logic diagram below





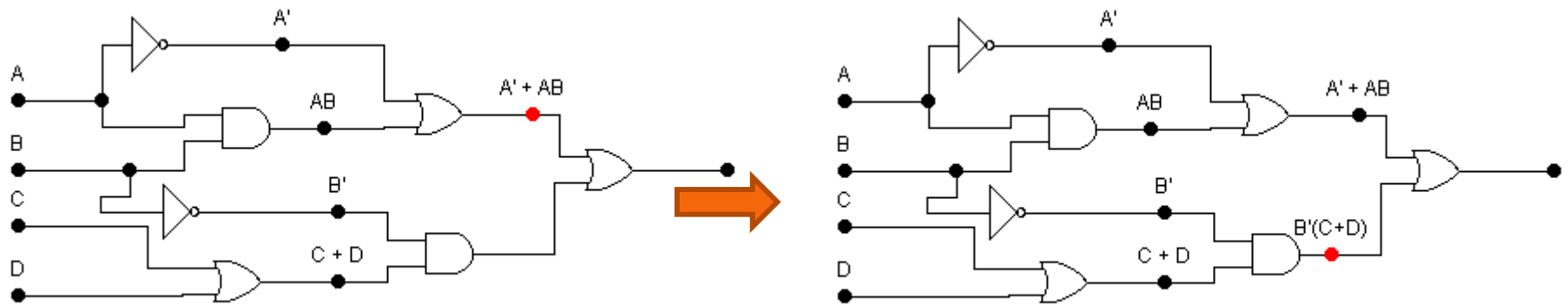

$$X = (\overline{A} + AB) + (\overline{B}(C + D))$$

$$X = (\overline{A} + B) + (\overline{B}(C + D))$$


$$X = (\overline{A} + B) + (\overline{B}C + \overline{B}D)$$

$$X = \overline{A} + B + \overline{B}C + \overline{B}D$$

$$X = \overline{A} + B + C + \overline{B}D$$



$$X = \overline{A} + B + C + \overline{B}D$$

$$X = \overline{A} + B + C + D$$

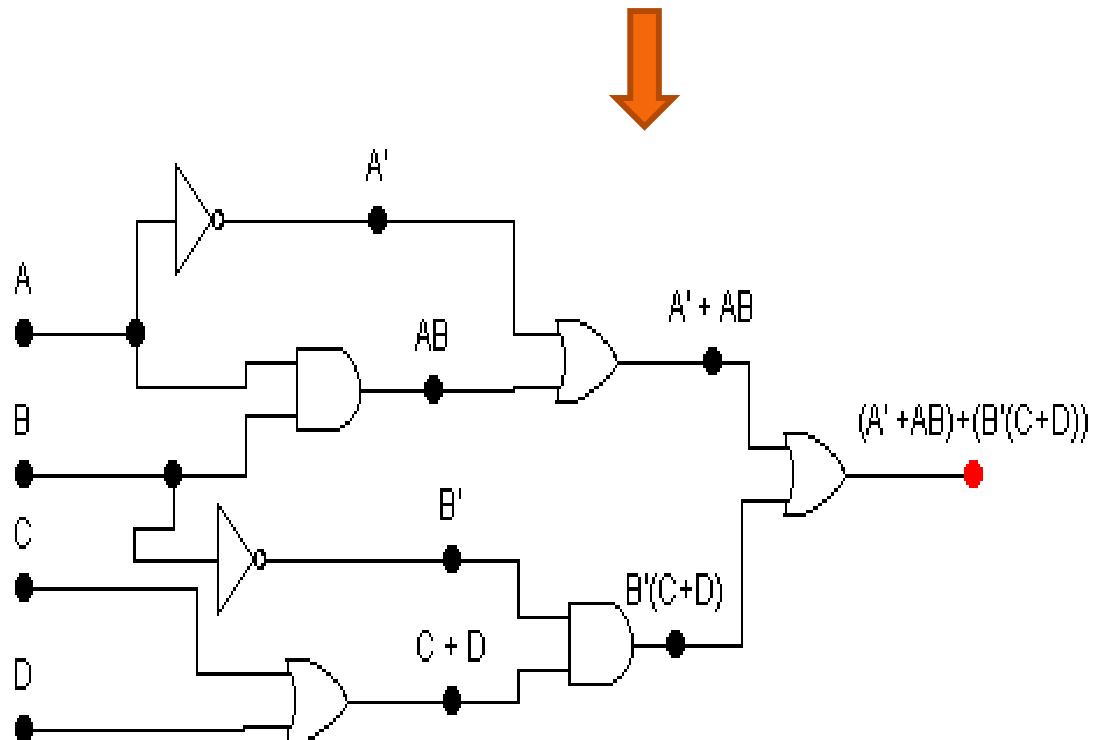

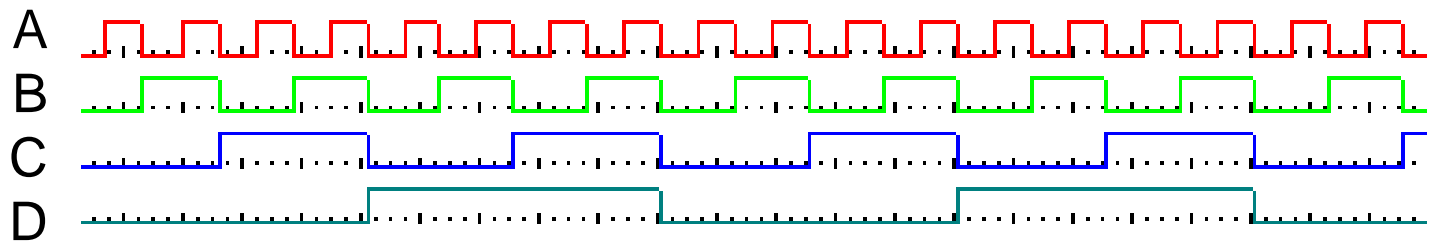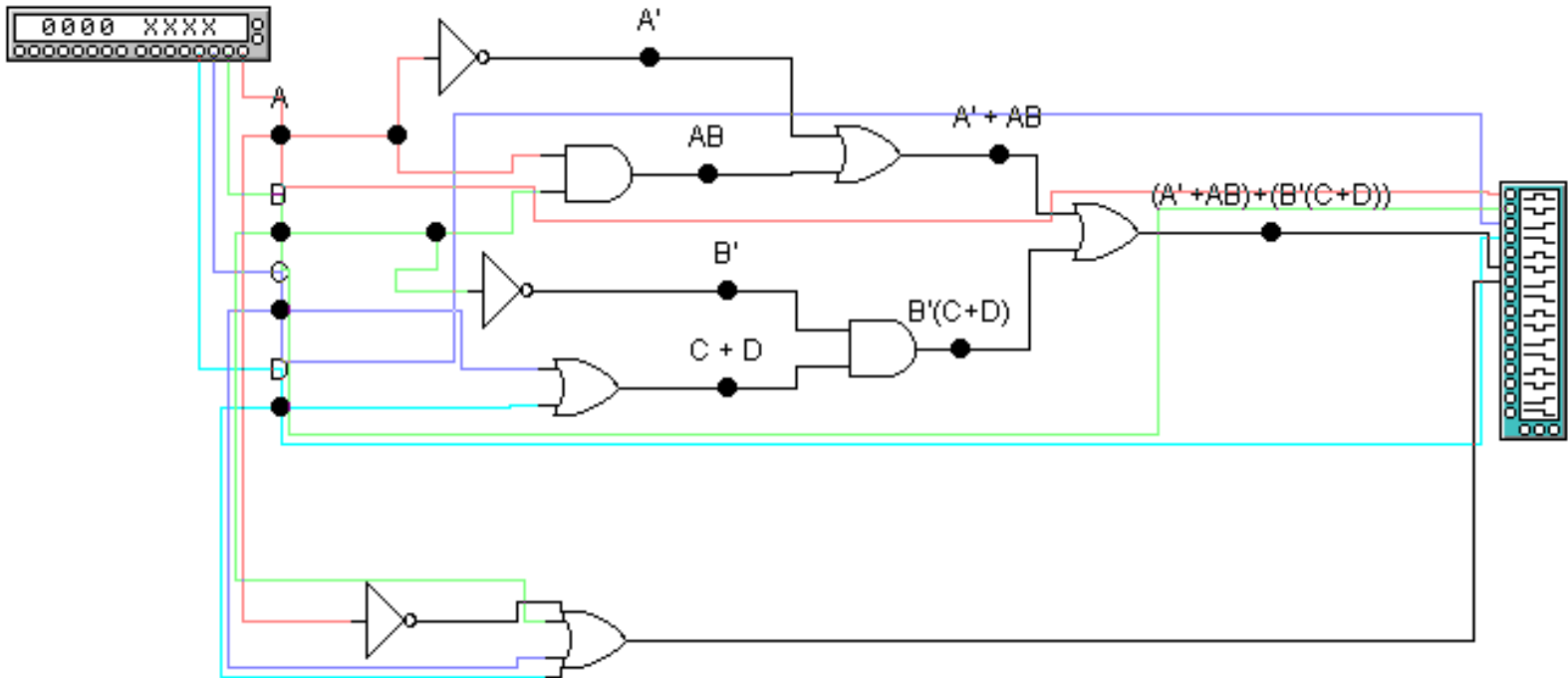
# Proof

∞ The circuits are different but the outputs are the same







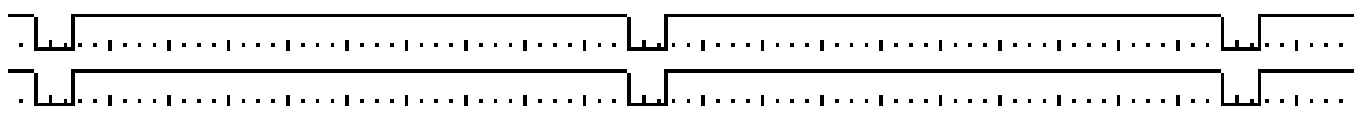
$(A' + AB) + (B'(C + D))$   
 $A' + B + C + D$



# Another simplification example




∞ Simplify the logic diagram below

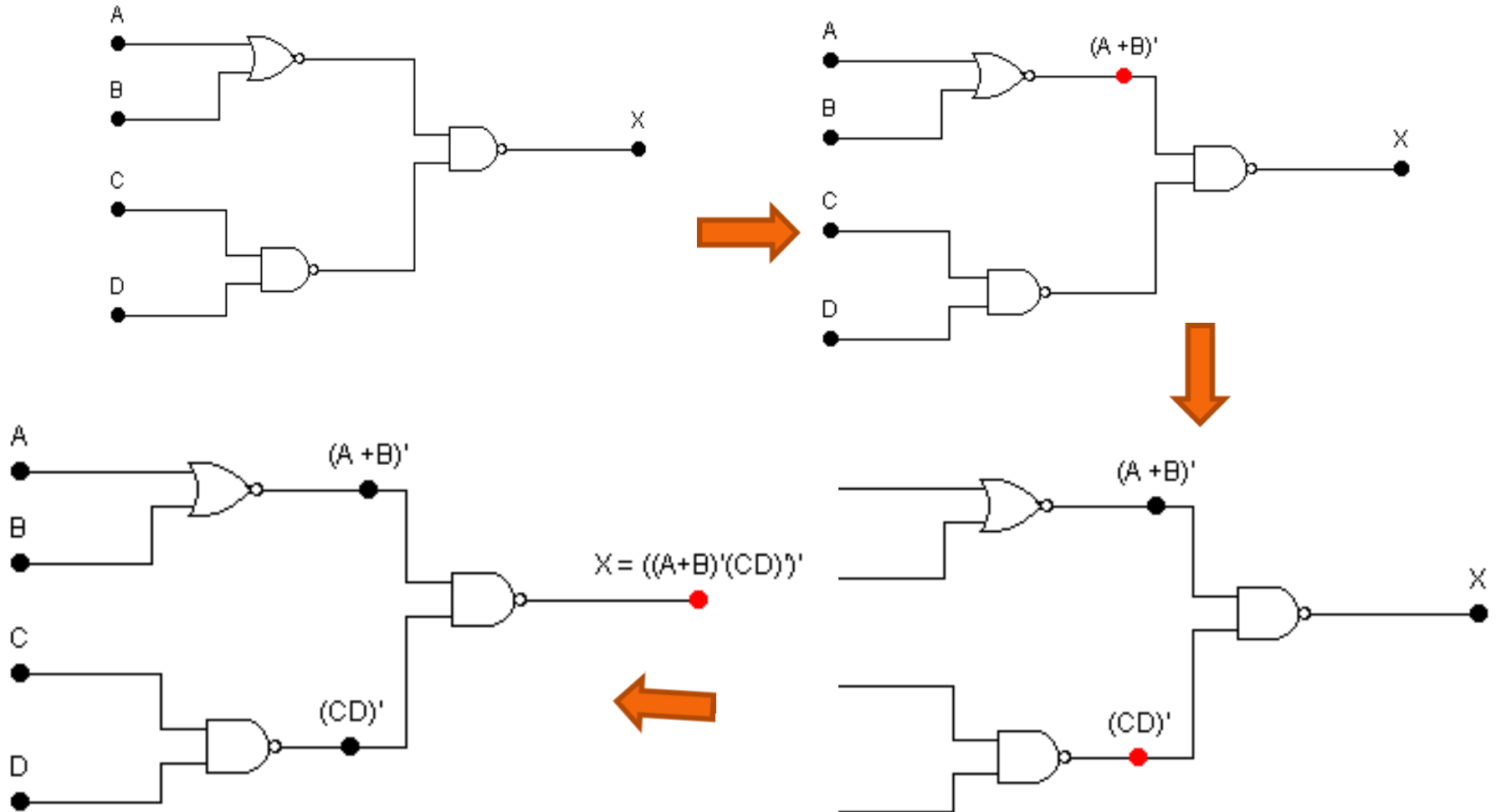

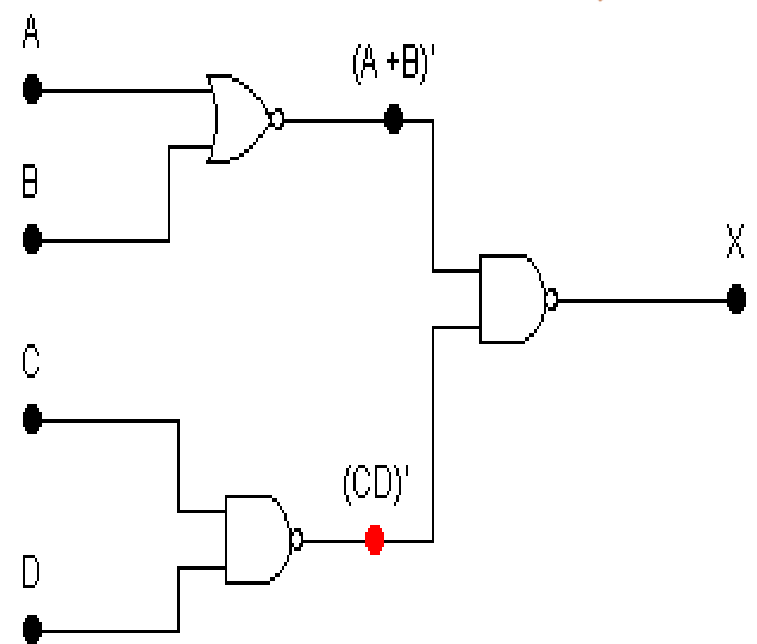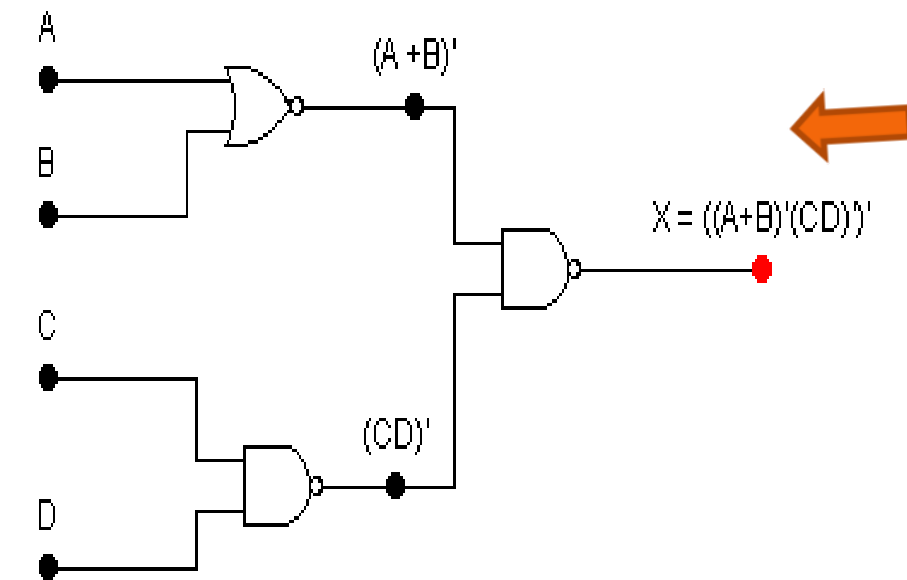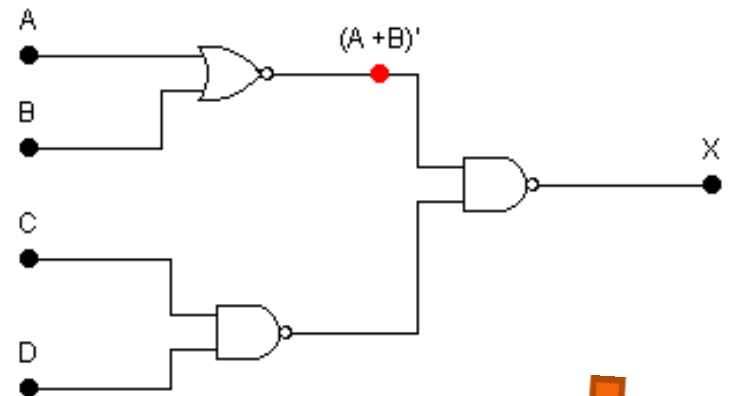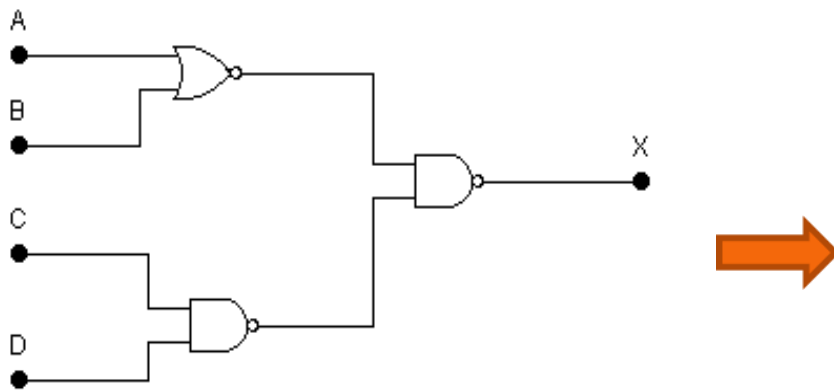

$$\begin{aligned}
 ((A + B)'(CD)')' &= \underline{\underline{(A + B)}} + \underline{\underline{CD}} \\
 &= A + B + CD
 \end{aligned}$$


# Proof

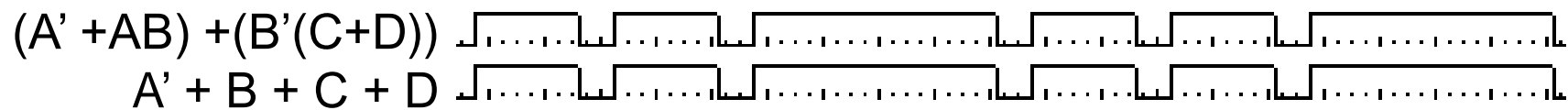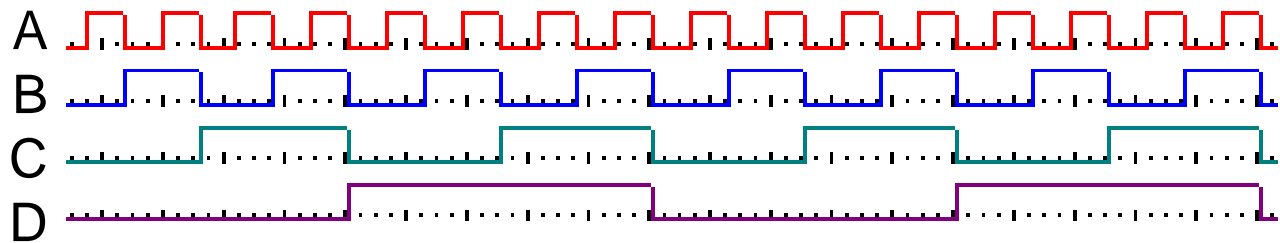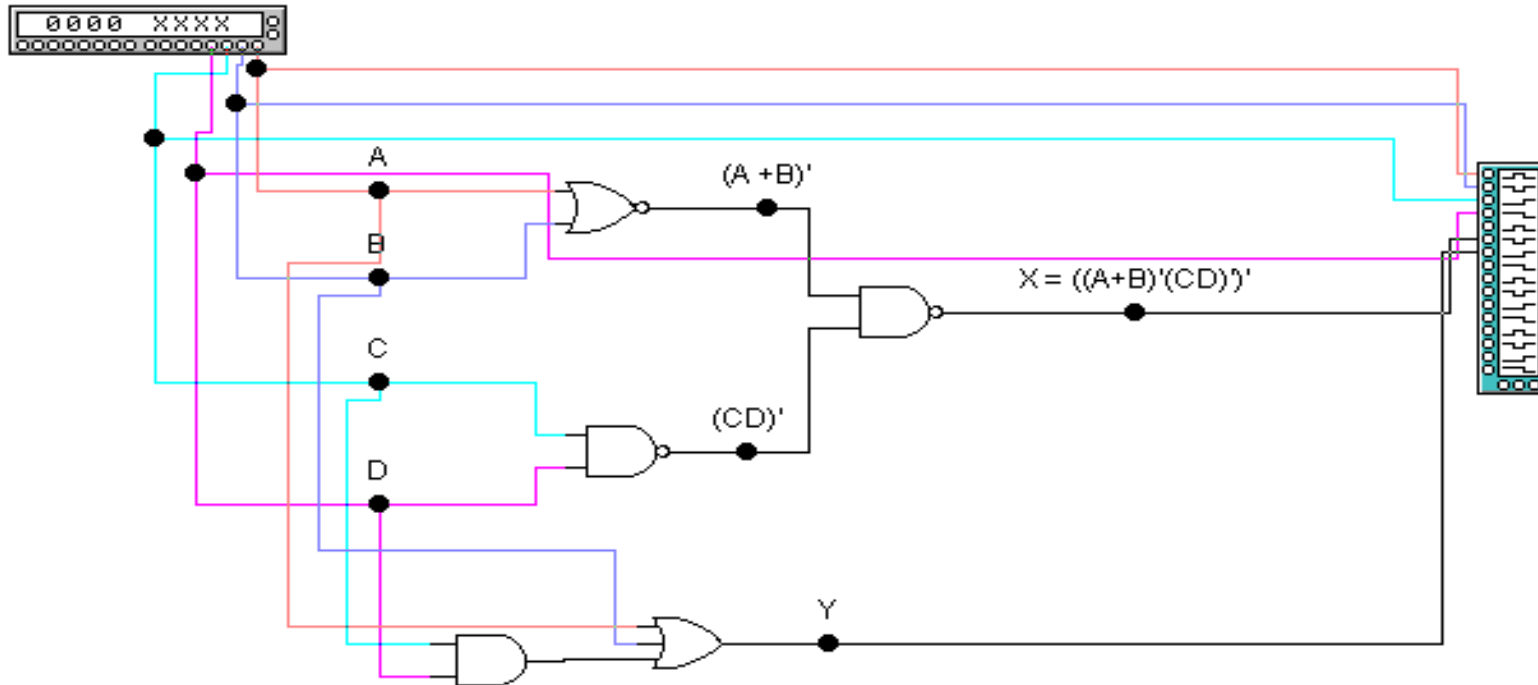

## Example 6

Draw the Logic circuit for the boolean expression Y


$$Y = [(A+B')'A][(B'+C)A] + [B'+C+B']$$

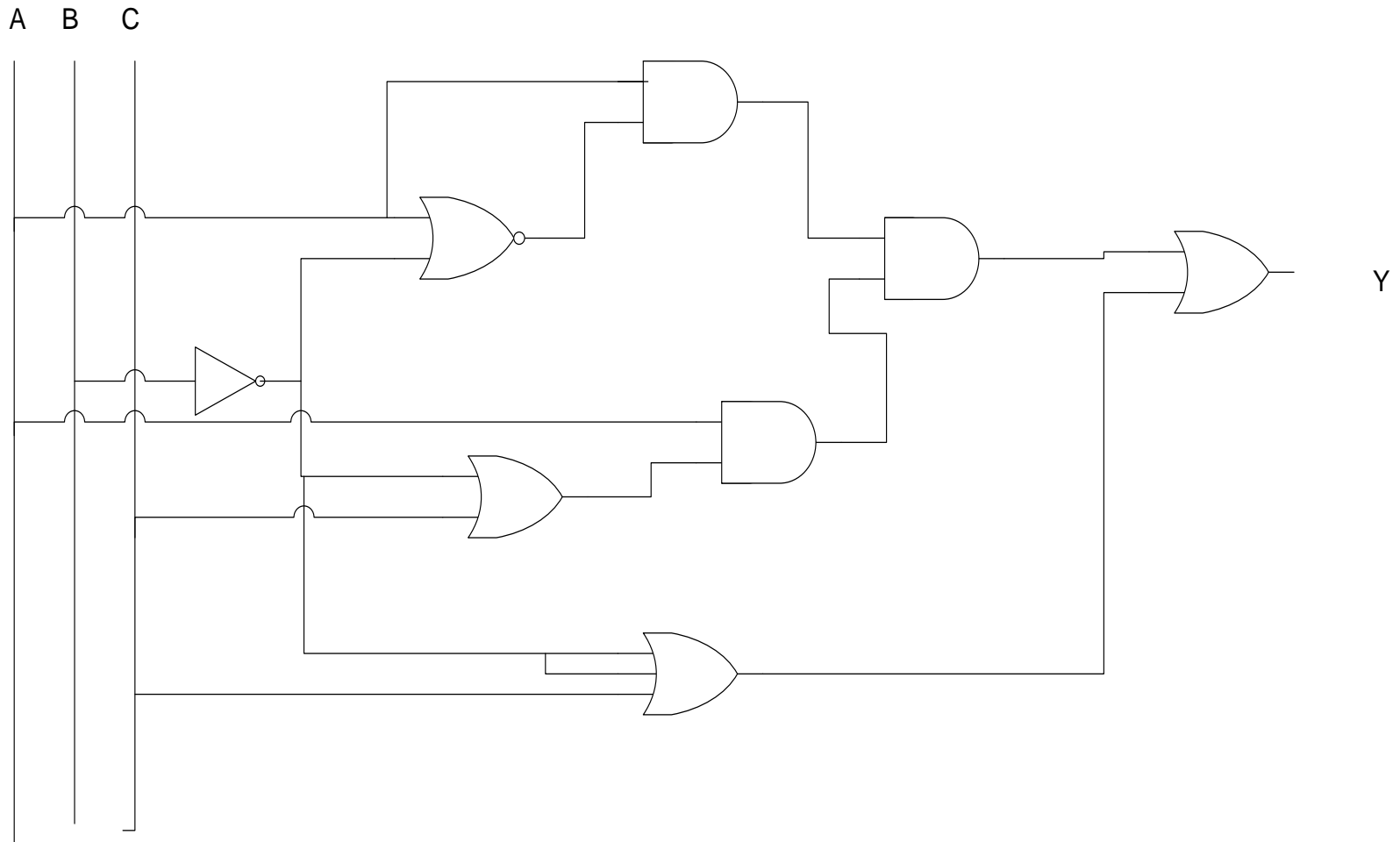
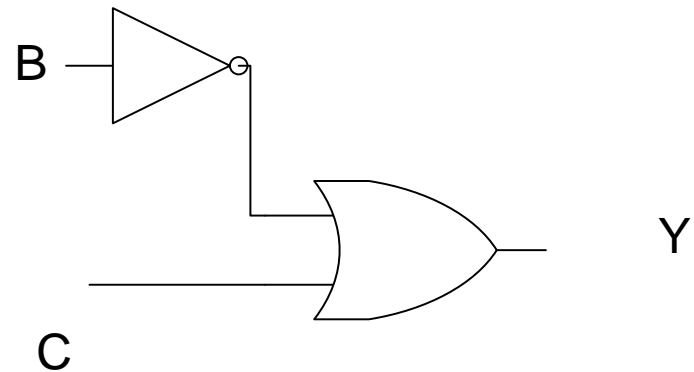
## Example 6

Simplify Y using boolean algebra rules + theorems and draw the resulting logic diagram for Y

$$\begin{aligned} Y &= \overline{(A + \bar{B})A}[(\bar{B} + C)A] + [\bar{B} + C + \bar{B}] \\ &= [\bar{A}\bar{\bar{B}}\bar{A}][A\bar{B} + AC] + [\bar{B} + C] \\ &= 0[A\bar{B} + AC] + [\bar{B} + C] \\ &= 0 + [\bar{B} + C] \\ &= \bar{B} + C \end{aligned}$$



# Truth tables

- Truth tables for boolean expressions are similar to truth tables for individual gates – each gate is individually evaluated, then combined (using boolean algebra) repeatedly until the output is achieved
- Example : Create the truth table for the given Boolean expression

$$Y = [(A+B')'A][(B'+C)A] + [B'+C+B']$$

INPUT						$X_1$		$X_2$			OUTPUT
A	B	C	$B'$	$A+B'$	$(A+B')'$	$(A+B')'A$	$B'+C$	$(B'+C)A$	$X_1X_2$	$B'+C+B'$	Y
0	0	0	1	1	0	0	1	0	0	1	1
0	0	1	1	1	0	0	1	0	0	1	1
0	1	0	0	0	1	0	0	0	0	0	0
0	1	1	0	0	1	0	1	0	0	1	1
1	0	0	1	1	0	0	1	1	0	1	1
1	0	1	1	1	0	0	1	1	0	1	1
1	1	0	0	1	0	0	0	0	0	0	0
1	1	1	0	1	0	0	1	1	0	1	1



# Validation

- ✂ The boolean expression earlier was simplified to  $Y = B' + C$
- ✂ Truth tables can be used to validate the simplification

INPUT						$X_1$		$X_2$			OUTPUT
A	B	C	$B'$	$A+B'$	$(A+B')'$	$(A+B')'A$	$B'+C$	$(B'+C)A$	$X_1X_2$	$B'+C+B'$	Y
0	0	0	1	1	0	0	1	0	0	1	1
0	0	1	1	1	0	0	1	0	0	1	1
0	1	0	0	0	1	0	0	0	0	0	0
0	1	1	0	0	1	0	1	0	0	1	1
1	0	0	1	1	0	0	1	1	0	1	1
1	0	1	1	1	0	0	1	1	0	1	1
1	1	0	0	1	0	0	0	0	0	0	0
1	1	1	0	1	0	0	1	1	0	1	1

# Summary

- ∞ The Boolean sum of two or more literals equivalent to an OR operation.
- ∞ The Boolean product of two or more literals equivalent to an AND operation
- ∞ Boolean algebra has its roots in conventional algebra → 12 rules in total
- ∞ Boolean expressions (and their corresponding logic diagrams) can be simplified using algebra rules and DeMorgan's theorems to create shorter expressions (and smaller logic diagrams)