

PDS0101

Introduction to Digital Systems

Latches & Flip-flops I

Lecture outcome


- ✧ By the end of today's lecture you should know
 - how basic gates combine to form latches
 - the operation of basic S-R, gated S-R and D latch
 - learn the difference between active HIGH and active LOW latches
 - identify the states of any latch and invalid con

Latches


- ∞ A latch is a temporary storage device that has two stable states – SET and RESET
 - Sometimes called *bistable logic device* or *multivibrator*
- ∞ They retain their states indefinitely until certain conditions change them
- ∞ Similar to flip-flops (to be covered later), latches reside in either of two states using a feedback style arrangement in which outputs are feedback to opposite inputs
- ∞ Latches begin the study of sequential logic which will later cummlate with counters and shift registers

Set-Reset (S-R) Latch

 
- Two types of S-R latch can be formed depending on the gates used
 - using two cross-coupled NOR gates - the latch responds to active-HIGH inputs
 - using two cross-coupled NAND gates - responds to active-LOW inputs




(a) Active-HIGH input S-R latch

 

 (b) Active-LOW input \bar{S} - \bar{R} latch




(a) Active-HIGH input
S-R latch

 

 (b) Active-LOW input
 \bar{S} - \bar{R} latch

Active-LOW S'-R' Latch


- Two NAND gates are cross-coupled so that the output of G1 is connected to one of the inputs of G2, and vice versa
- There are two latch inputs
 - the SET input is the input that **sets Q to the 1 state**.
 - The CLEAR input is the input that **resets Q to the 0 state**
- The gate outputs, labeled Q and Q', respectively, are latch outputs.
- Under normal conditions, the outputs will always be the inverse of each other



Note: the following diagrams show the RESET input as CLEAR



Active-LOW S'-R' Latch

 - ∞ An alternative to using two NAND gates is to use two negative-OR gates (this is the example shown in the textbook)



S'-R' latch – resting state

  - ∞ In a resting/stable state, the inputs S' and R' are normally in HIGH state




- ∞ Assuming that $Q=0$ (and thus $Q'=1$), inputs to G2 are 0 and 1 which produce $Q'=1$ (because NAND) so Q' remains high
- ∞ With $Q'=1$, both inputs to G1 are high and produce $Q=0$
- ∞ Conversely, if $Q=1$ and $Q'=0$, the output would be similar but inversed with Q maintaining a high output and Q' a low
 - In effect, with both inputs S and R at high, the outputs remain unchanged from the state they are currently in

S'-R' latch – resting state

- Summary of condition SET = 1 and CLEAR = 1.
 - There are two possible output states when SET and RESET = 1, which are either $Q = 0$ and $Q' = 1$ or $Q = 1$ and $Q' = 0$.
 - The outputs are remain unchanged comparing with previous state even there is new clock pulse or new input $S = 1$ and $R = 1$
- To change the state of the S'-R' latch, one of the inputs will be pulsed LOW whenever we want to change the latch outputs


S'-R' latch – SET state

 - ∞ In the SET state, the S input is made low (because active-LOW)
- ∞ Assuming that the current state of the latch was from resting, the following occurs



- ∞ As S is pulsed to LOW, Q will go HIGH ($Q=1$) and this causes both inputs to G2 to become HIGH and causes Q' to go LOW
- ∞ Thus the latch ends up with $Q=1$ and $Q'=0$

 
- ∞ If prior to input S being made LOW the outputs were $Q=1$ and $Q'=0$ (i.e. the latch is already in SET state), the following occurs:



- ∞ You can see that the LOW input to G1 does not affect the output of the latch and it remains SET
- ∞ Summary of condition $SET = 0$ and $RESET = 1$.
- A LOW input on SET will always cause the latch to end up in the $Q = 1$ state and $Q' = 0$.
 - This operation is called *setting the latch*


S'-R' latch – RESET state

 - ∞ To switch the ALS-R latch to RESET (i.e resetting the latch), the R input is made LOW
- ∞ If the current state is SET, the following occurs



- ∞ When R is LOW, both inputs to G2 now result in a HIGH output $Q'=1$
- ∞ Both inputs to G1 are now HIGH and result in an output $Q=0$ thus resetting the latch



 
- ☞ If prior to input R being made LOW the outputs were $Q=0$ and $Q'=1$ (i.e. the latch is already in RESET state), the following occurs:



- ☞ As before, the LOW input to G2 does not affect the output of the latch and it remains RESET
- ☞ Summary of condition $SET = 1$ and $RESET = 0$.
- A LOW pulse on the RESET input will always cause the latch to end up in the $Q = 0$ state and $Q' = 1$.
 - This operation is called clearing or resetting the latch



S'-R' latch – invalid state

   - When SET and RESET inputs are simultaneously made LOW, this will produce HIGH levels at both NAND output, $Q = 1$ and $Q' = 1$ and violating the complement nature of the outputs
 - This condition occurs no matter what state the latch was currently in
- This is an undesired condition because the two outputs are supposed to be inverses of each other





- ✎ When in invalid state, if both input LOWs are released (made HIGH) simultaneously both outputs will attempt to go LOW and thus propagating the invalid state.
- ✎ In reality, there is always *some* miniscule difference in the propagation time delay at the gates so one of the gates will dominate in its transition to the LOW (or HIGH) output state → the slower gate will then always be forced to be complement
 - In this scenario, you can NOT predict the next state of the latch


S'-R' latch – state summary

  

  
(a) Two possibilities for the SET operation



 (b) Two possibilities for the RESET operation



(c) No-change condition

 


(d) Invalid condition

S	R	Q
1	1	No change/resting
0	1	Q=1 and Q'=0
1	0	Q=0 and Q'=1
0	0	Invalid/unpredictable



S'-R' Latch Example

 - Assuming that $Q = 0$ initially, determine the output Q for the NAND S'-R' latch inputs shown below





Active HIGH S-R latch

  - Two cross-coupled NOR gates can be used as a active HIGH S-R latch (also known as a NOR gate latch)
- The arrangement is similar to the NAND latch except the Q and Q' outputs have reversed position against the inputs (i.e. $S \rightarrow Q'$ and $R \rightarrow Q$)




S-R latch – resting state

  - ∞ In a resting/stable state, the inputs S and R are normally in LOW state
→ the latch remains in whatever state it is currently in/started with




S-R latch – SET state

 - ∞ The S-R latch moves into a SET state when the S input is made HIGH
- ∞ If the initial state was SET, the latch remains as SET




S-R latch – RESET state

 - ∞ The S-R latch moves into RESET state when the R input is made HIGH
- ∞ If the initial state was RESET, the latch remains as SET



S-R latch – invalid state

 - Similar to the S'-R' latch, the S-R latch also encounters an invalid state but this time when both inputs to S and R are HIGH simultaneously




S-R latch – state summary

R	S	Q	Action
0	0	Last value	No change
0	1	1	Set
1	0	0	Reset
1	1	–	Invalid condition


Gated latch

 - ∞ A gated latch (either S-R or S'-R') adds another input – ENABLE – to basically turn the latch 'on' or 'off'
- ∞ The following shows the gated S-R latch logic diagram and symbol




(a) Logic diagram

opposing bubbles
cancel each other
out!!

 


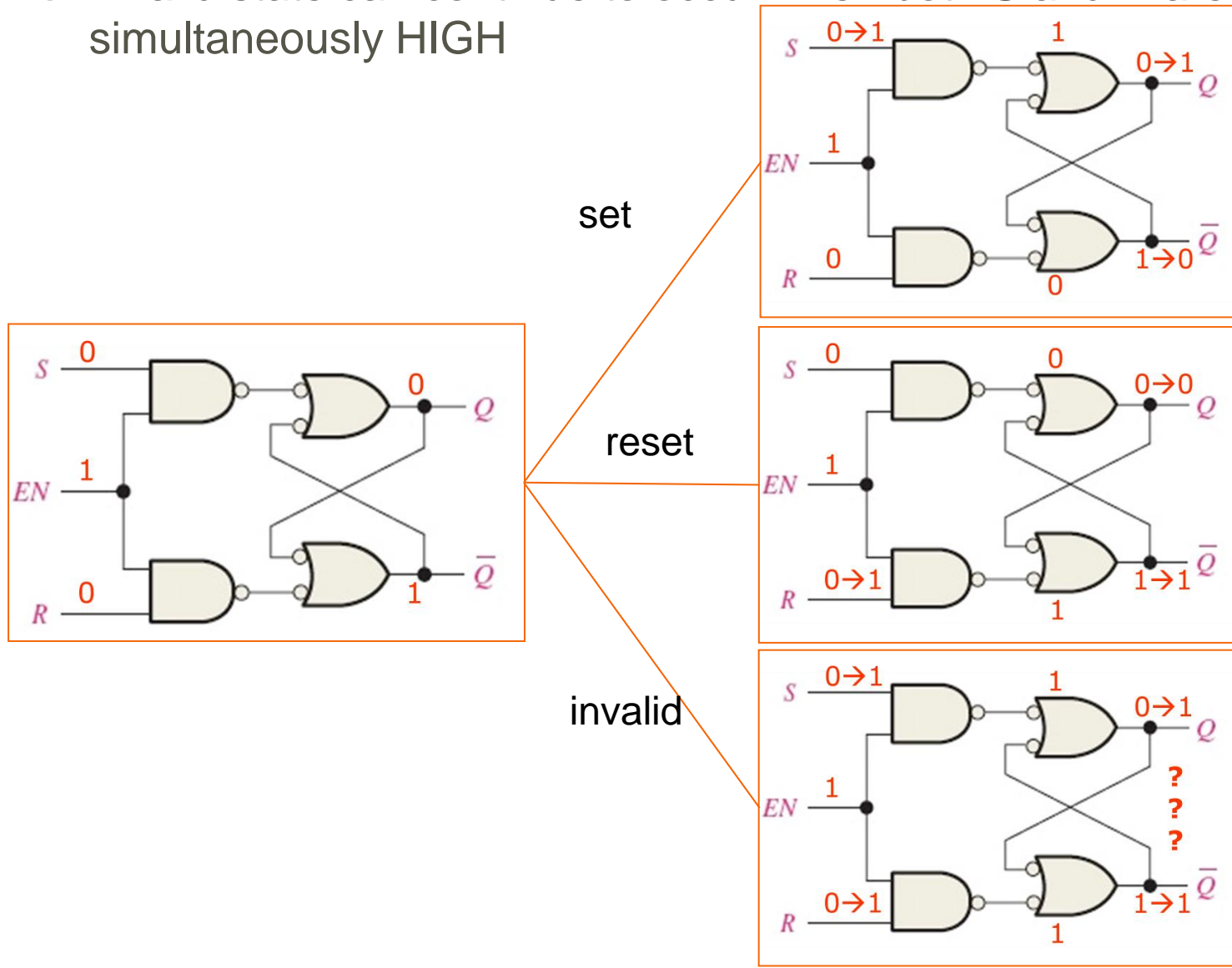(b) Logic symbol

- ✂ In the gated latch shown, the latch will not change until EN is HIGH (=1)
- ✂ As long as EN=1, the output is controlled by the S and R inputs
 - Invalid state can continue to occur when both S and R are simultaneously HIGH




Gated S-R latch timing diagram

 


Gated D latch

- ∞ A variant of the gated latch is called the D latch
 - only has two inputs – EN for enable and D for data
 - when EN and D inputs are HIGH, the latch will set
 - when EN and D inputs are LOW, the latch will reset
 - There is no invalid condition since it is not possible to set both inputs to the latch gates to HIGH simultaneously
- ∞ A simple rule for the *D* latch is: *Q follows D when the Enable is active.*


 


D latch timing diagram

 


  Exercise

- Draw the resulting Q output waveform of the latches below. Assume that Q state starts LOW




 - Repeat the process with the inputs S and R below



 
Exercise

- ✧ Using the latch shown, determine outputs Q and Q' assuming that Q starts LOW



 
Exercise

- For a gated D latch, the waveforms below are used at the inputs D and EN . Draw the resulting timing diagram showing the output waveform you would expect to see at Q if the latch is initially RESET




Summary

 
- ✧ A latch forms a temporary storage device which retains its state until it is explicitly changed by its input signal (control)
- ✧ Latches can be in two states – SET and RESET
- ✧ The S-R and gated S-R latch has invalid condition
- ✧ Logic symbols for all the latches covered




(a) Active-HIGH
input S-R latch

 

 (b) Active-LOW input
 \bar{S} - \bar{R} latch



(c) Gated S-R latch

 

(d) Gated D latch