

PDS0101

Introduction to Digital Systems


Logic Gates

Lecture outcome

- ✧ By the end of today's lecture you should know
 - Common logic gates used in digital systems
 - Symbols used to represent logic gates in circuits
 - The boolean algebra equivalency of each gate
 - Basic differences with PLD and FLD components


Logic Gates

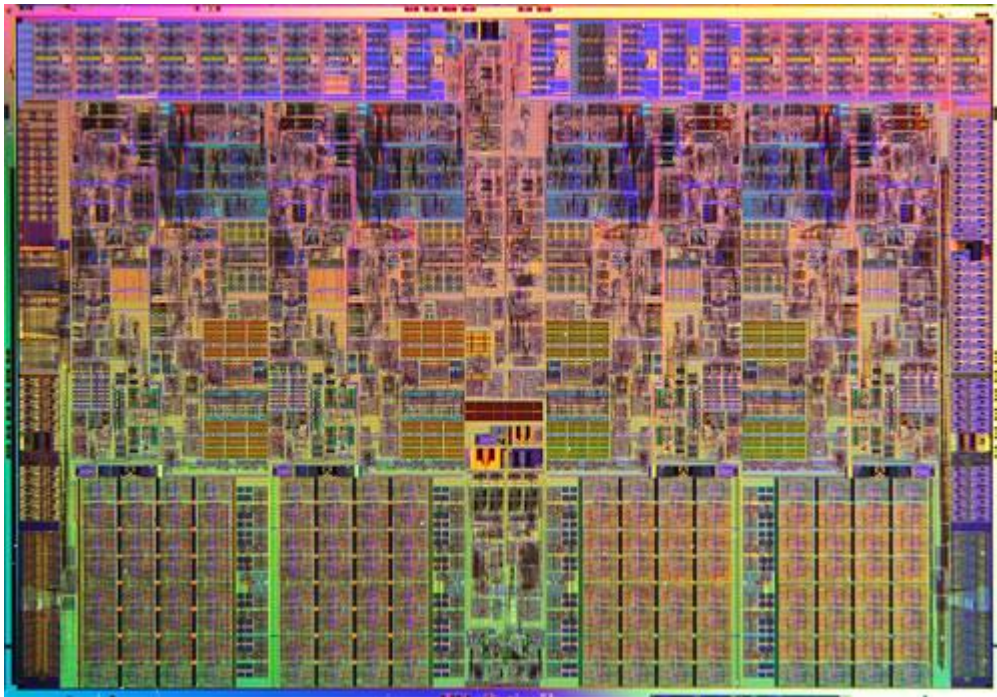- ∞ Logic gates are the building blocks of computers
- ∞ Most of the functions in a computer, with the exception of certain types of memory, are implemented with logic gates used on a very large scale
- ∞ For example, a microprocessor, which is the main part of the computer, is made of up of hundreds of thousands of logic gates




The Inverter

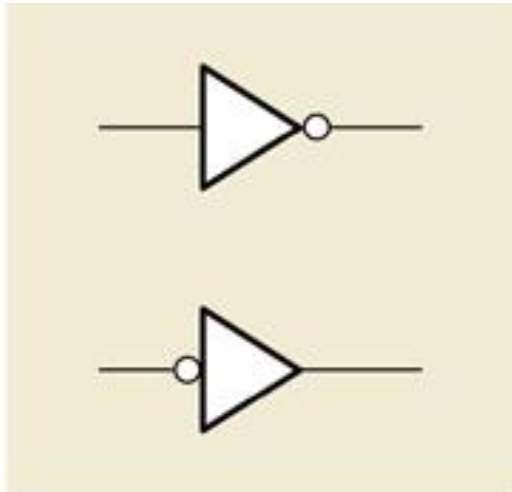- ∞ The Inverter (NOT circuit) performs the operation called inversion or complementation.
- ∞ The inverter changes one logic level to the opposite level. In terms of bits, it changes a 1 to a 0 and a 0 to 1
- ∞ The symbol for a NOT circuit, which is more commonly called INVERTER:



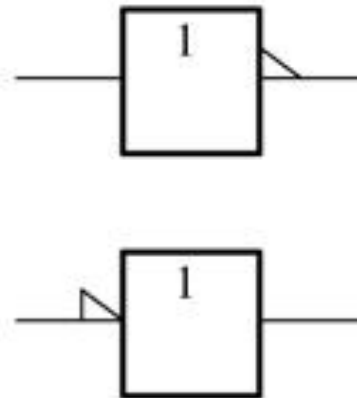
(a) Distinctive shape symbols with negation indicators





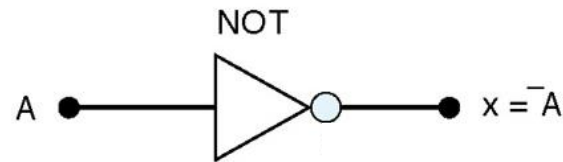
(b) Rectangular outline symbols with polarity indicators

The Inverter

- ∞ This circuit always has only a single input and its output logic level is always opposite to the logic level of this input




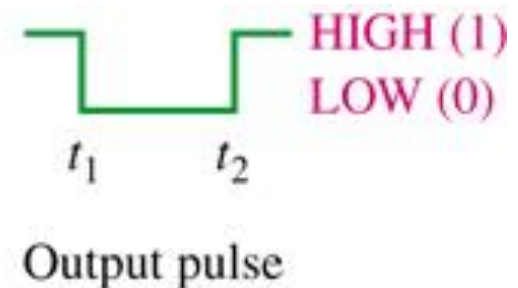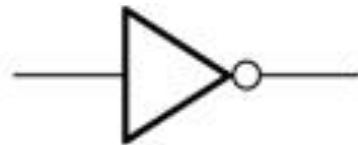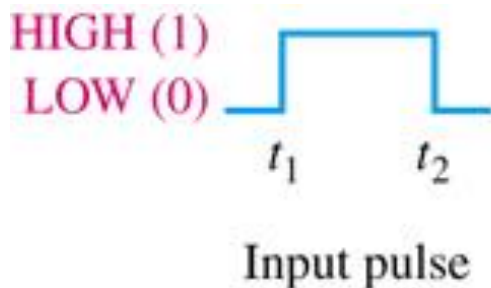- ∞ When the input is LOW, the output is HIGH; when the input is HIGH, the output is LOW, thereby producing an inverted output pulse.



Inverter truth table

Input A	Output $X = \bar{A}$
Low (0)	High (1)
High (1)	Low (0)

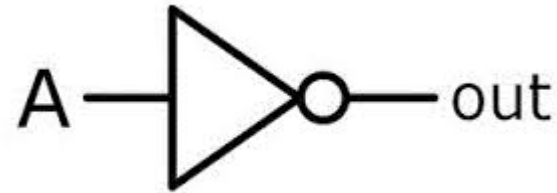


Boolean Equation Output = $\overline{\text{Input}}$
 $X = \bar{A}$




The AND gate

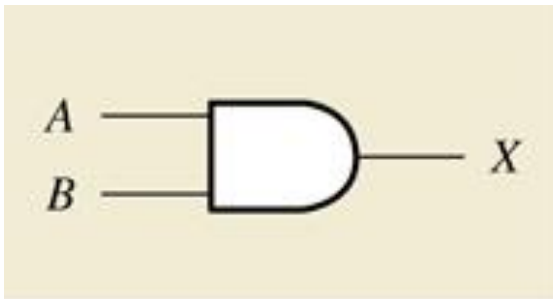- ∞ The AND gate is one of the basic gates that can be combined to form any logic function
- ∞ An AND gate can have two or more inputs and performs what is known as logical multiplications
- ∞ The AND gate is a circuit that operates in such a way that its output is HIGH only when ALL its inputs are HIGH.
- ∞ For all other cases the AND gate output is LOW



(a) Distinctive shape

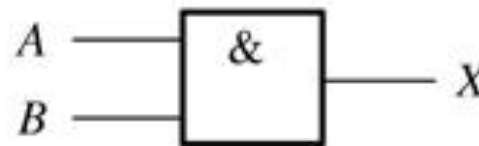

(b) Rectangular outline
with the AND (&
qualifying symbol

- ∞ The AND gate output is equal to the AND product of the logic inputs; that is $x=AB$


The AND gate

∞ All possible logic levels for a 2-input AND gate.



AND gate truth table



Input A	Input B	Output (AB)
Low (0)	Low (0)	Low (0)
Low (0)	High (1)	Low (0)
High (1)	Low (0)	Low (0)
High (1)	High (1)	High (1)

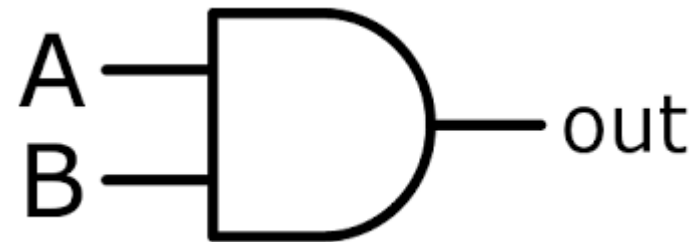

Boolean Equation $X = AB$

AND Timing diagram

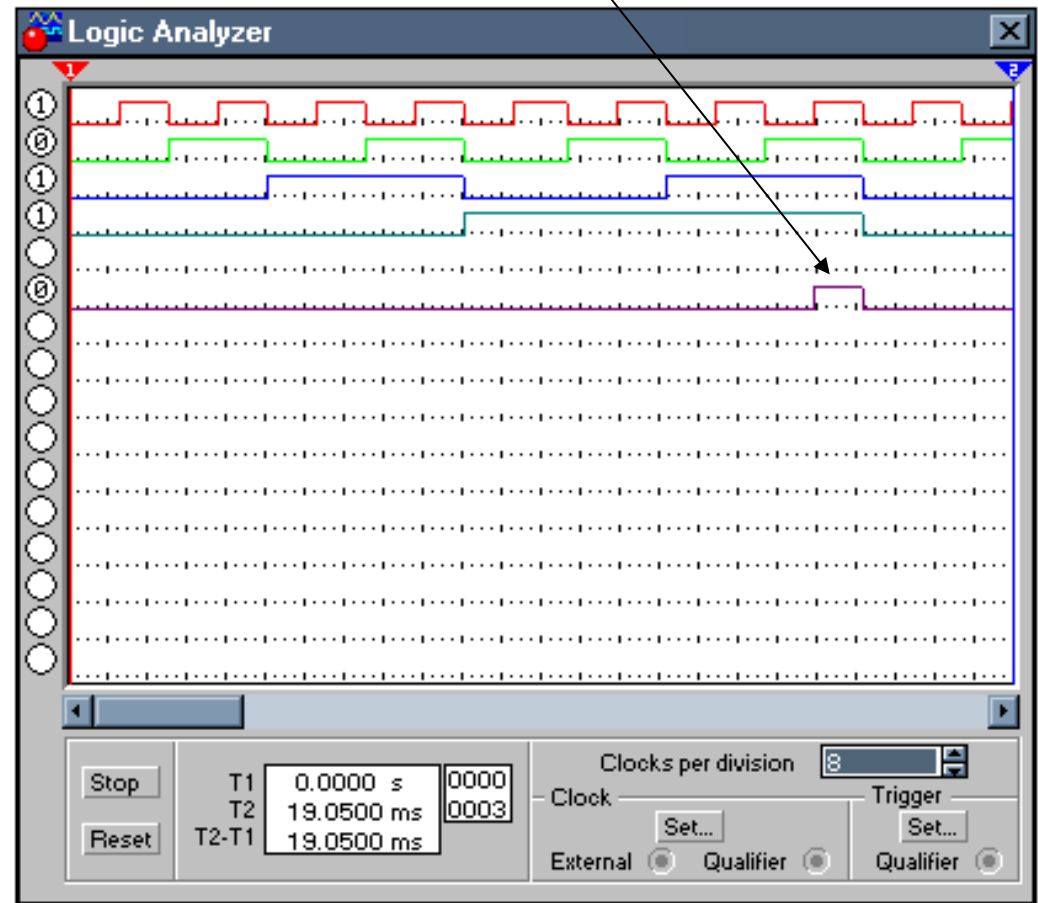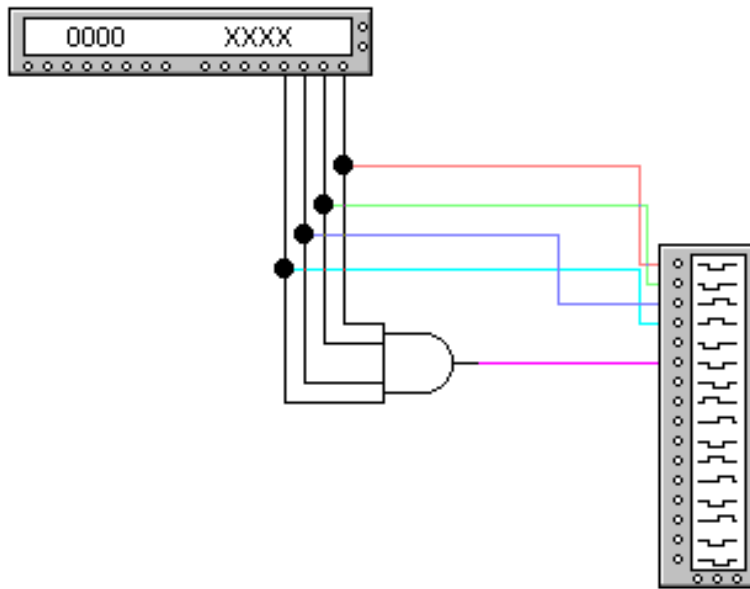All inputs must be high for the output to be high



Problem solving


1. Develop the truth table for a 3-input AND gate.
2. Determine the total number of possible input combinations for a 4-input AND gate.
3. What is the only input combination that will produce a HIGH at the output of the five-input AND gate?

Summary of the AND operation


- ∞ The AND operation is performed the same as ordinary multiplication of 1s and 0s.
- ∞ An AND gate is a logic circuit that performs the AND operation on the circuit's inputs.
- ∞ An AND gate output will be 1 only for the case when all inputs are 1; for all other cases the output will be 0.
- ∞ The expression $x=AB$ is read as “x equal A AND B”.

The OR gate

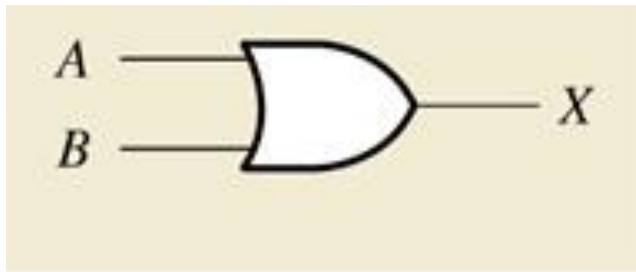- ✧ It can have any number of inputs greater than one.
- ✧ An OR gate produces a HIGH on the output when any of the inputs is HIGH.
- ✧ The output is LOW only when ALL inputs are LOW.
- ✧ Therefore OR gate determines when one or more inputs are HIGH and produces a HIGH on its output to indicate this condition.




(a) Distinctive shape

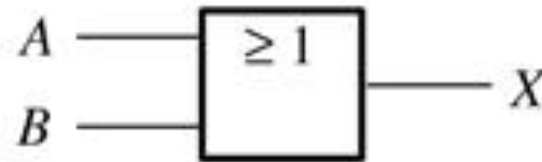

(b) Rectangular outline
with the OR (≥ 1)
qualifying symbol

OR gate truth table

Input A	Input B	Output X = A+B
Low (0)	Low (0)	Low (0)
Low (0)	High (1)	High (1)
High (1)	Low (0)	High (1)
High (1)	High (1)	High (1)

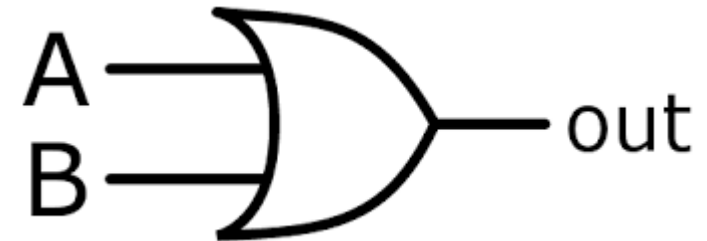

Boolean Equation $X = A+B$

Boolean addition is the same as the OR function

$$0 + 0 = 0$$


$$0 + 1 = 1$$

$$1 + 0 = 1$$


$$1 + 1 = 1$$

OR Timing diagram


All must be low for the output to be low

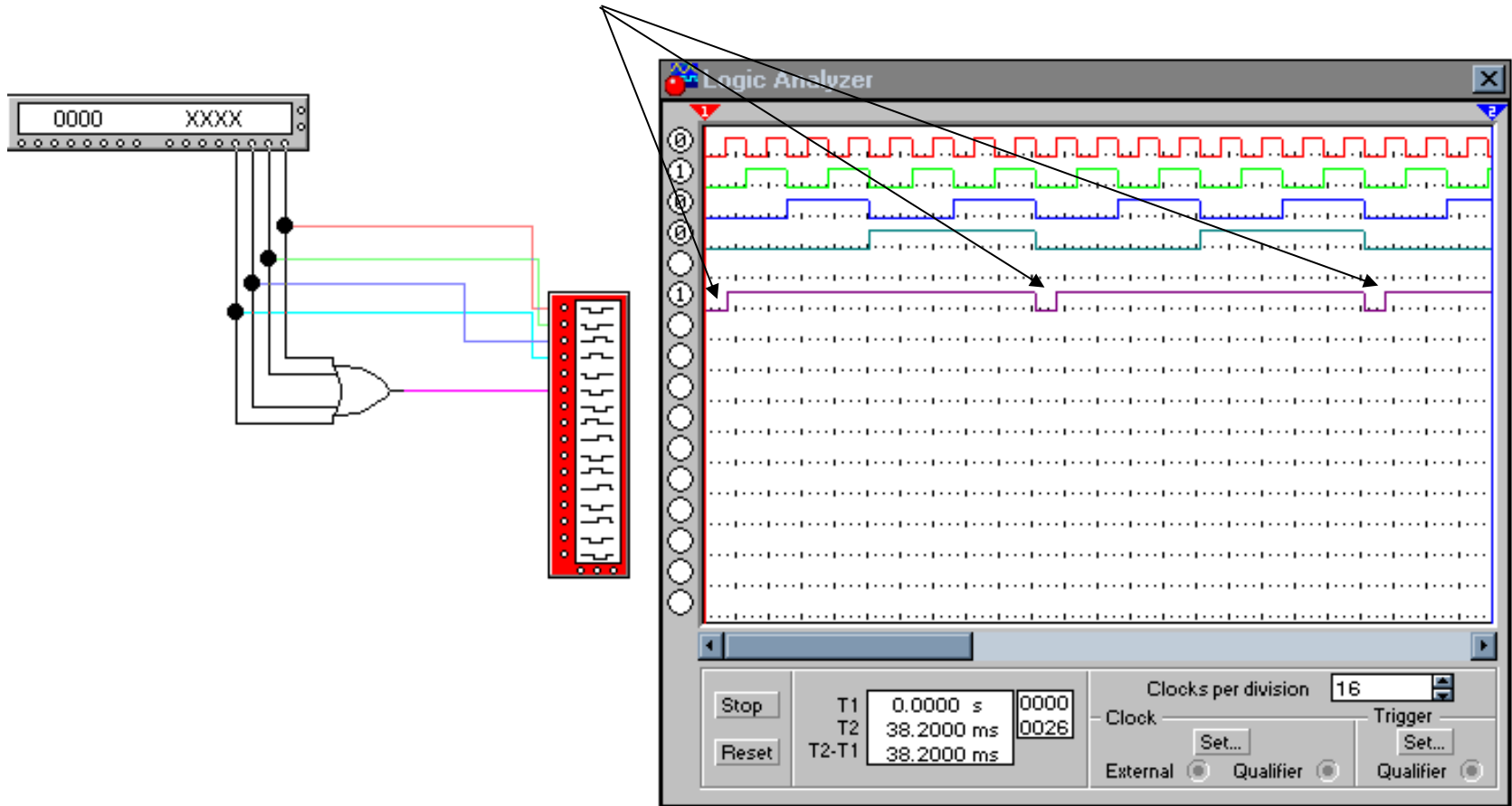

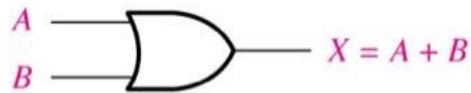
- ∞ The operation of a 2-input OR gate can be expressed as follows:
 - if one input variable is A, if the another input variable is B, then output variable is $X = A + B$
- ∞ Figure shows boolean expressions for OR gates with two, three, and four inputs



(a)

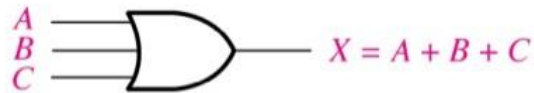

(b)

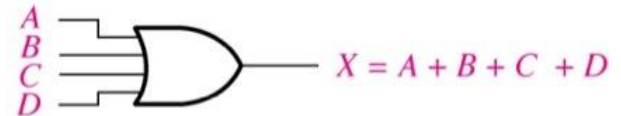


(c)


The NAND gate

∞ The NAND operates like an AND gate followed by an INVERTER

$$X = \overline{AB}$$

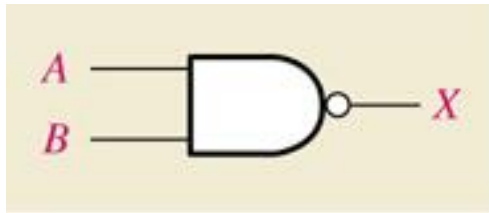


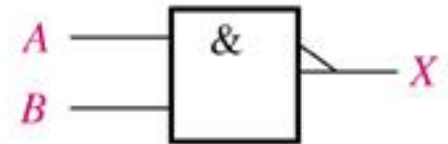
(a) Distinctive shape, 2-input NAND gate and its NOT/AND equivalent



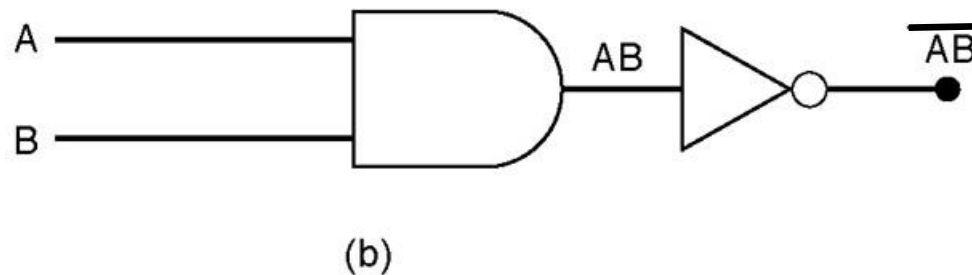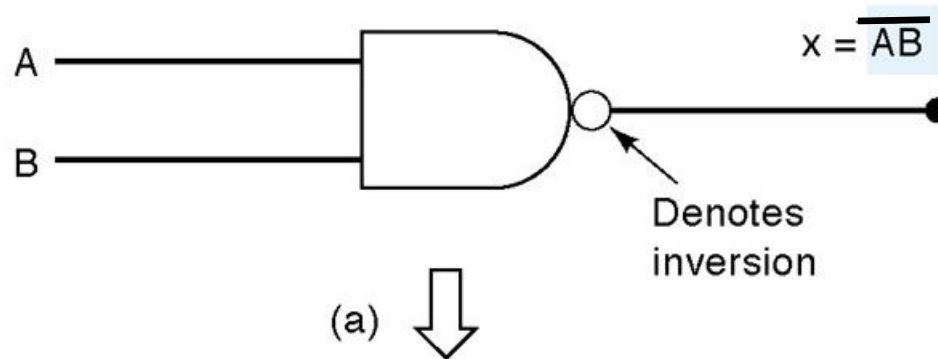(b) Rectangular outline, 2-input NAND gate with polarity indicator

The NAND gate

- ✎ The symbol for a 2 input NAND gate is shown in fig; It is same as the AND gate symbol except for the small circle on its output




		AND		NAND	
A	B	AB		\overline{AB}	
0	0	0		1	
0	1	0		1	
1	0	0		1	
1	1	1		0	

(c)

- ✎ Once again this small circle in front denotes the inversion operation.

NAND gate truth table



Input A	Input B	Output (\overline{AB})
Low (0)	Low (0)	High (1)
Low (0)	High (1)	High (1)
High (1)	Low (0)	High (1)
High (1)	High (1)	Low (0)

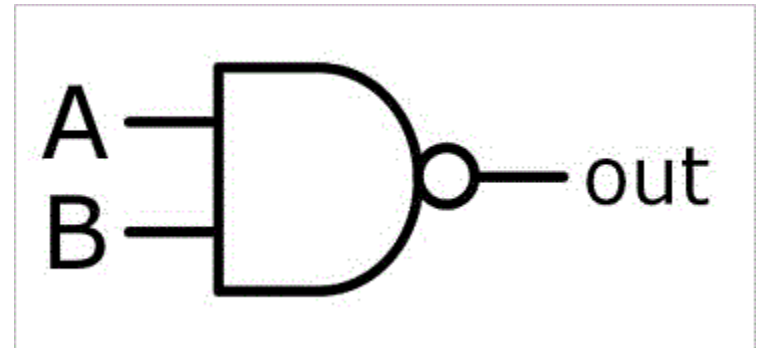

Boolean Equation $X = \overline{AB}$

NAND Timing diagram


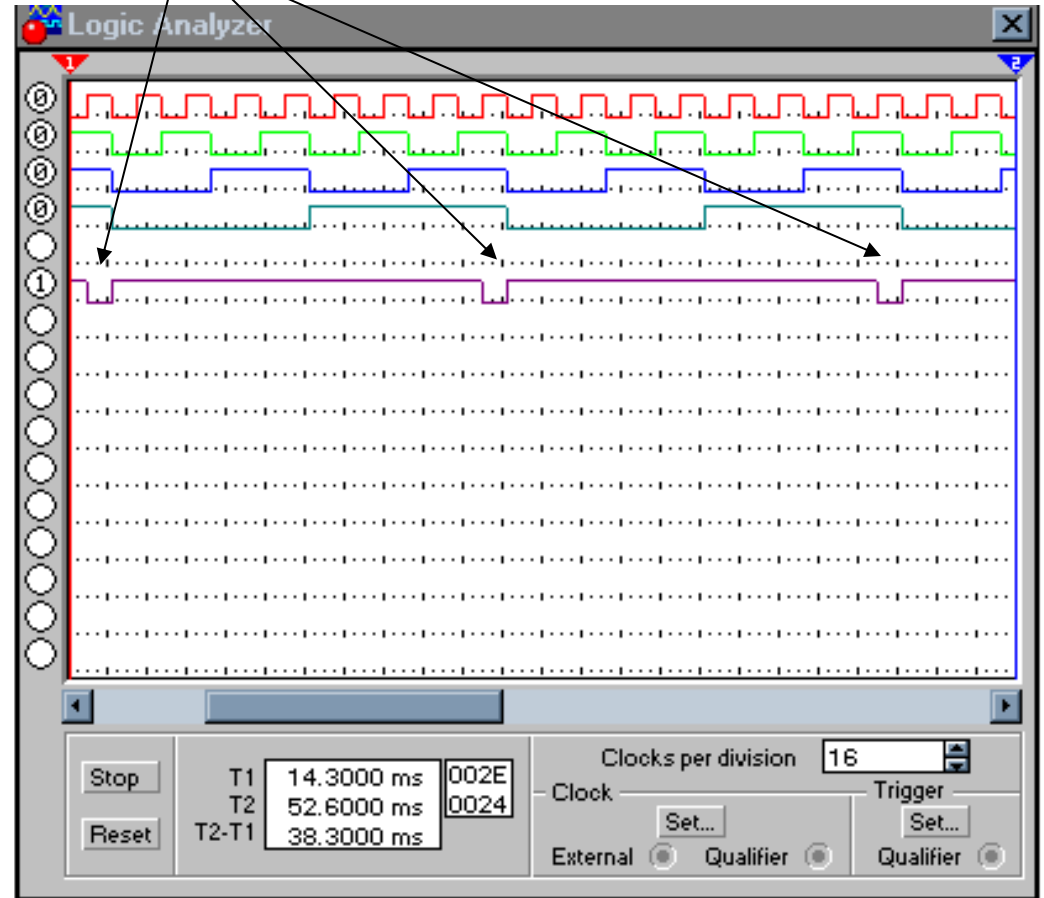
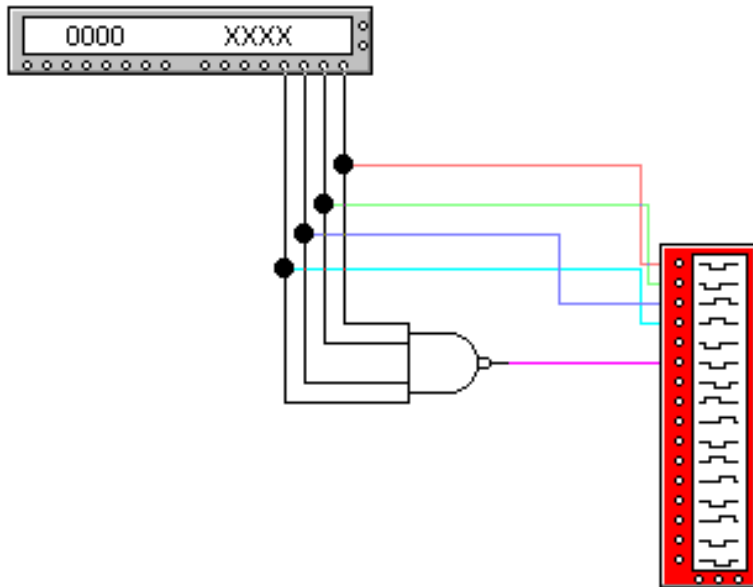
All inputs must be high for the output to be low



The NOR gate

∞ The NOR operates like an OR gate followed by an INVERTER.

$$X = \overline{A+B}$$

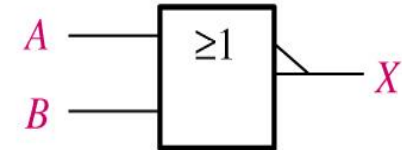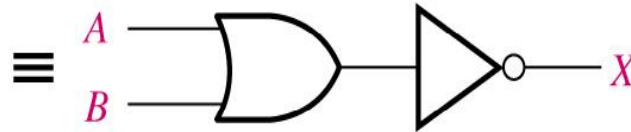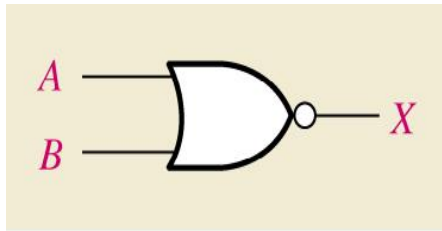


(a) Distinctive shape, 2-input NOR gate and its NOT/OR equivalent

(b) Rectangular outline, 2-input NOR gate with polarity indicator

NOR gate truth table


Input A	Input B	Output ($\overline{A+B}$)
Low (0)	Low (0)	High (1)
Low (0)	High (1)	Low (0)
High (1)	Low (0)	Low (0)
High (1)	High (1)	Low (0)

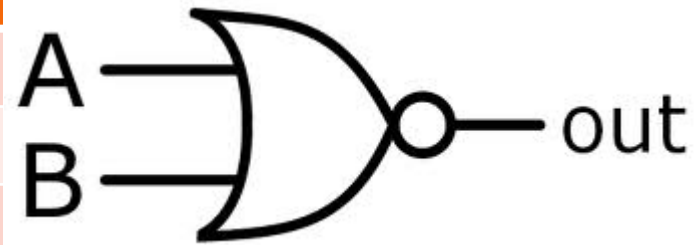


Boolean Equation $X = \overline{A+B}$

NOR Timing diagram

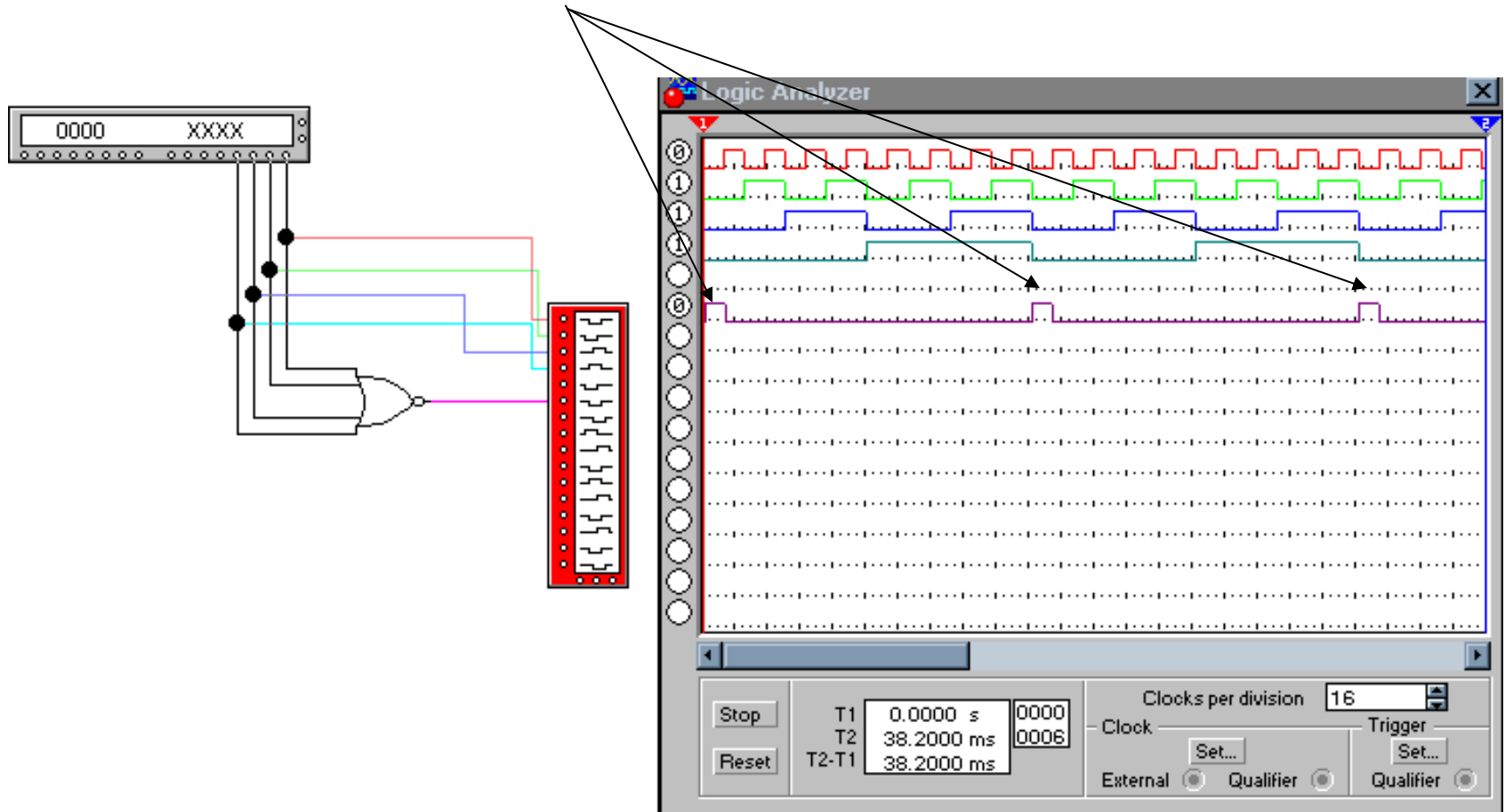
All inputs must be low for the output to be high



The Exclusive -OR gate

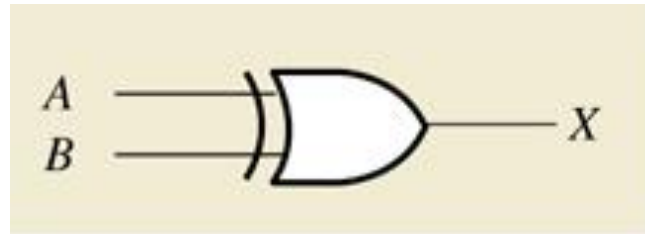


(a) Distinctive shape

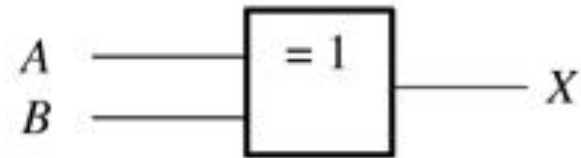

(b) Rectangular outline with the XOR qualifying symbol ($= 1$)

Exclusive-OR gate truth table

Input A	Input B	Output ($A \oplus B$)
Low (0)	Low (0)	Low (0)
Low (0)	High (1)	High (1)
High (1)	Low (0)	High (1)
High (1)	High (1)	Low (0)


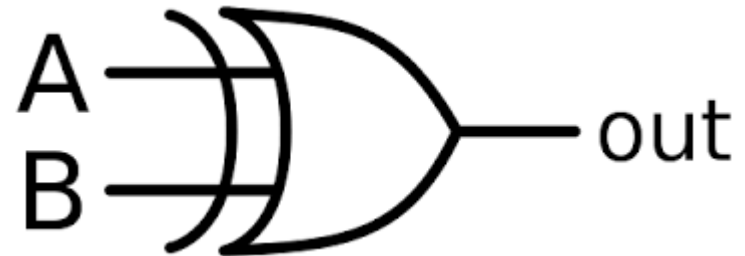


Boolean Equation $X = \overline{A}B + A\overline{B} = A \oplus B$

n/b: the output is shown High if and only if the total numbers of the input “High” is in odd number


Exclusive-OR Timing diagram

The 2 input exclusive-OR is less busy

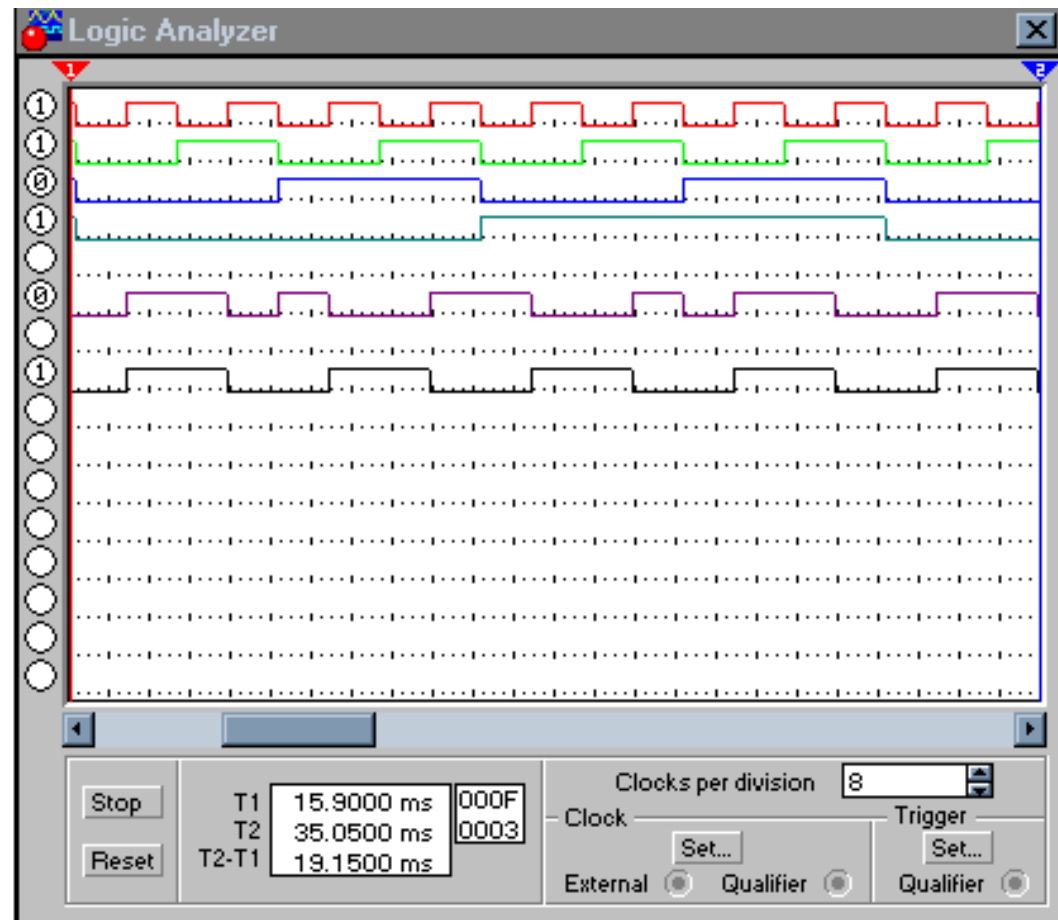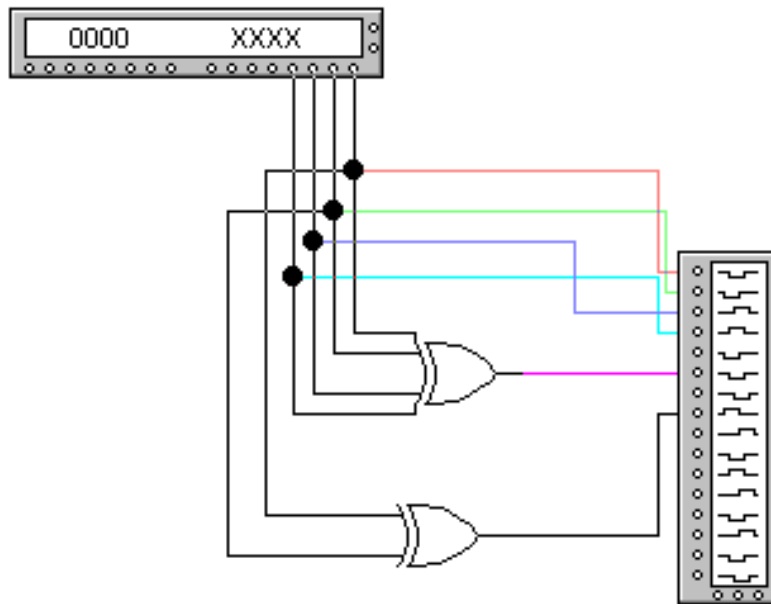


The Exclusive-NOR gate

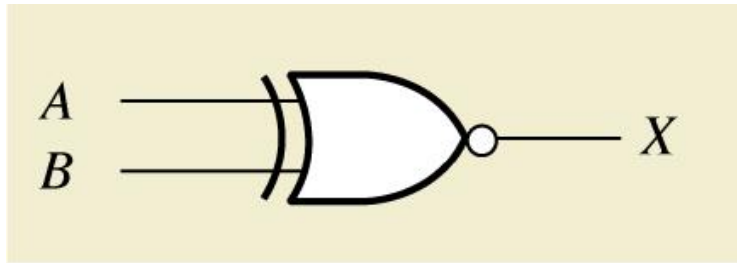- ∞ The output to the XNOR gate is high when both inputs A and B are high and when neither A nor B is high




(a) Distinctive shape

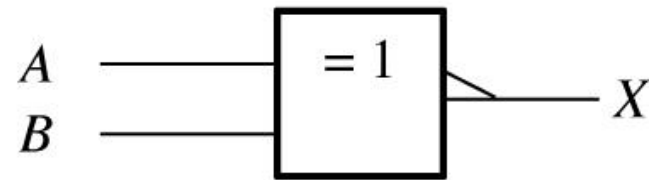

(b) Rectangular outline



Exclusive-NOR gate truth table

Input A	Input B	Output ($A \oplus B$)
Low (0)	Low (0)	High (1)
Low (0)	High (1)	Low (0)
High (1)	Low (0)	Low (0)
High (1)	High (1)	High (1)

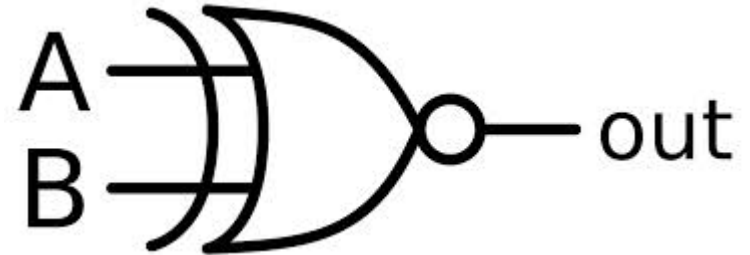

$$\begin{aligned}\text{Boolean Equation } X &= \overline{\overline{A}B + A\overline{B}} \\ &= AB + \overline{A}\overline{B} \\ &= \overline{A \oplus B}\end{aligned}$$

Exclusive-NOR Timing diagram

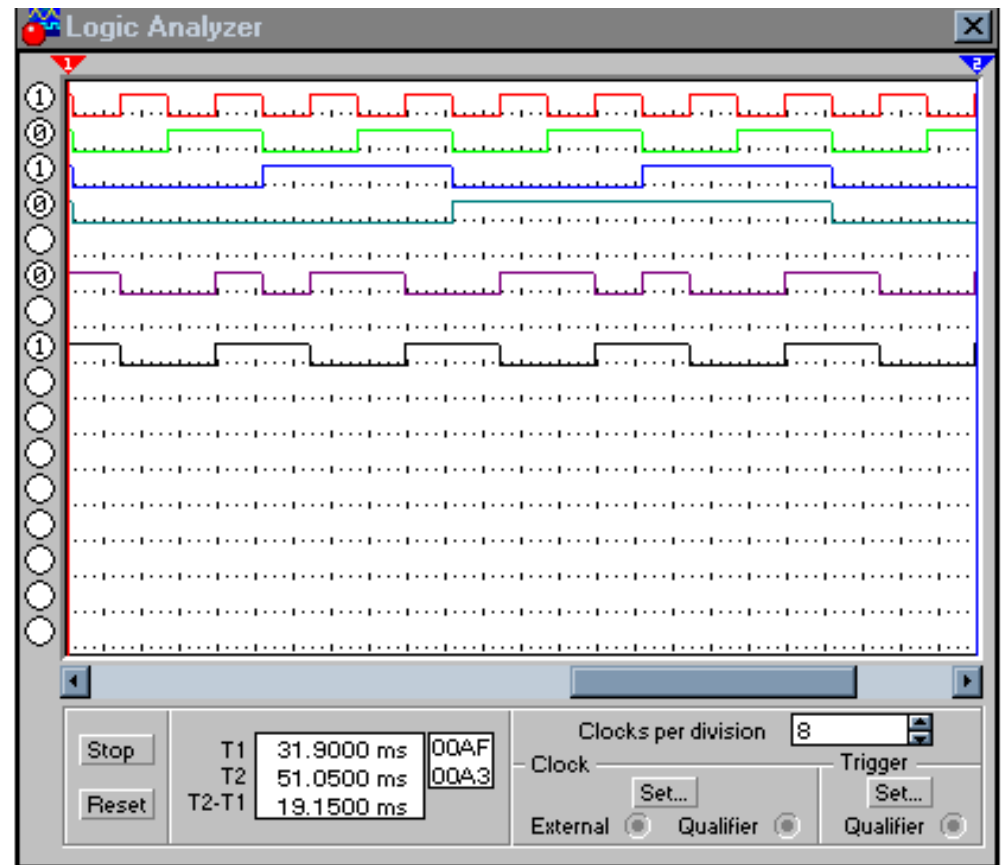
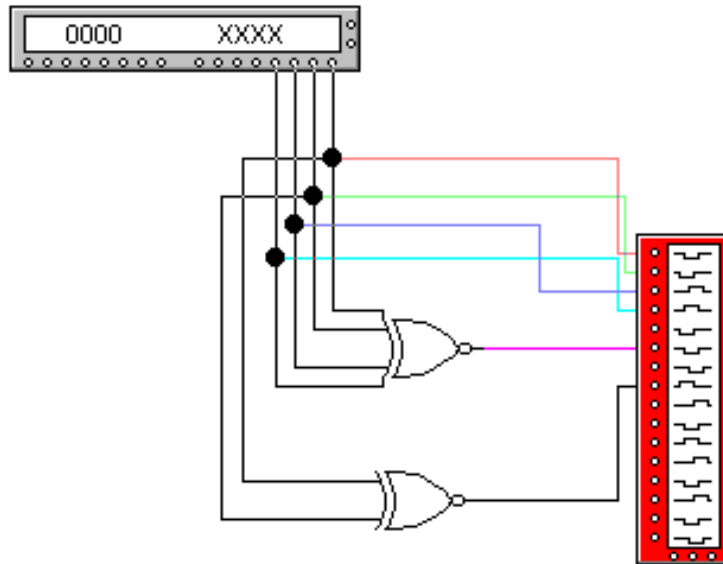


Logic devices


- ∞ Logic devices can be classified into two broad categories
- ∞ Fixed Function Logic Devices
 - Fixed logic devices are permanent, the specific logic function is contained in the IC package when it is purchased and it can never be changes “hard-wired”
- ∞ Programmable Logic Devices (PLD)
 - One in which the logic function is programmed by the user and can be programmed many times
 - PLDs can be changed at any time to perform different functions.

Fixed function logic

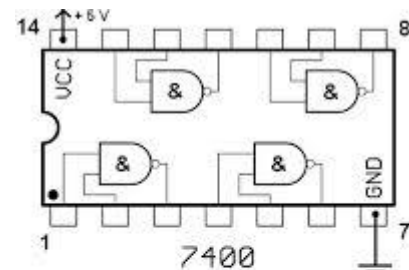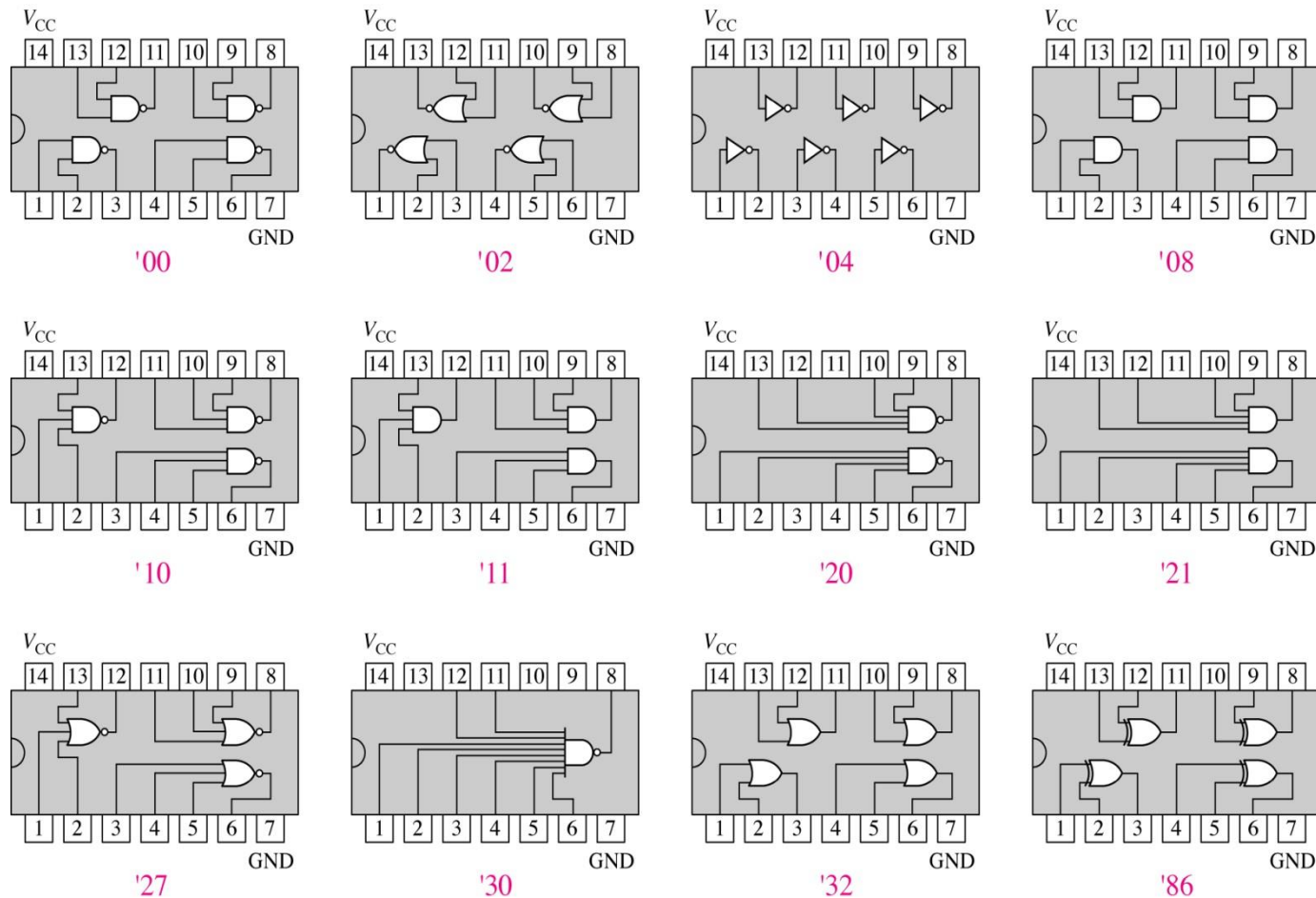
∞ Pin configuration diagrams for some common fixed-function IC gate configurations.





DIP and SOIC packages

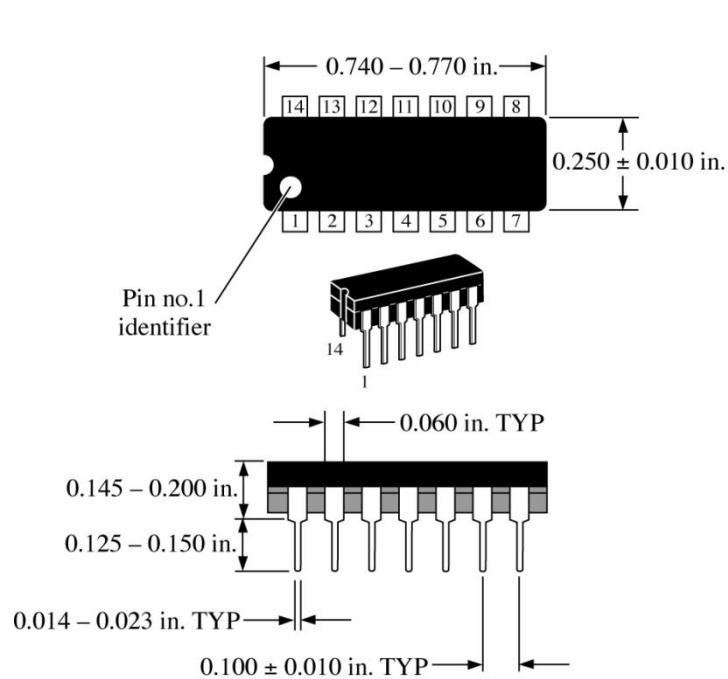

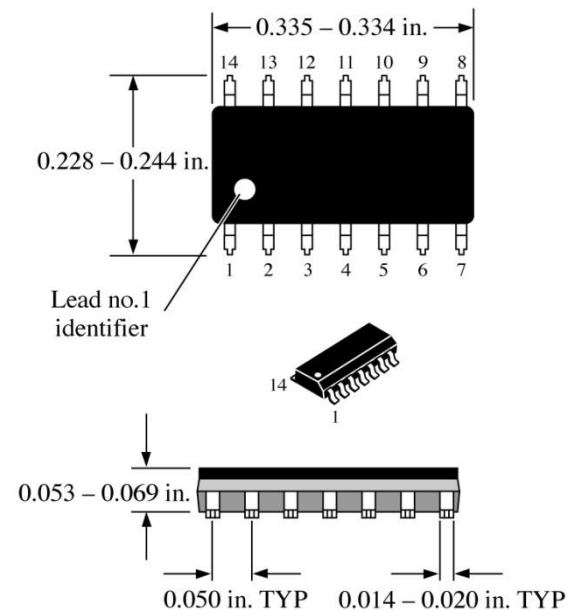(a) 14-pin dual in-line package (DIP) for feedthrough mounting



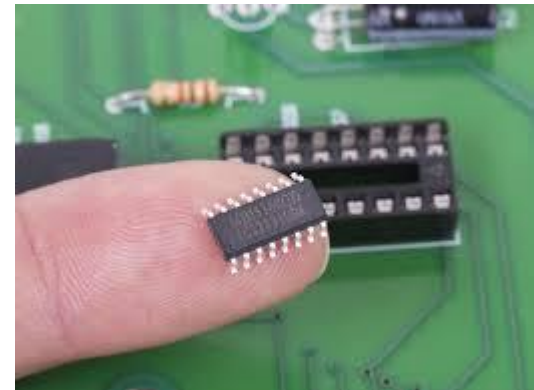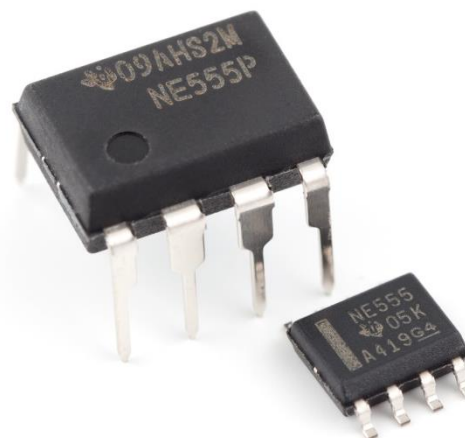(b) 14-pin small outline package (SOIC) for surface mounting






Programmable Logic Devices (PLD)

- ∞ The Another category of logic devices is one in which the logic function is programmed by the user and , in some cases , can be reprogrammed many times. These devices are called Programmable Logic Devices (PLD)
- ∞ Advantages of PLDs over Fixed function logic devices
- ∞ Many more logic circuits can be “stuffed” into a much smaller area with PLD
- ∞ Logic designs can be changed without rewiring or replacing components
- ∞ PLD design can be implemented faster than one using fixed function ICs once the required programming language is mastered

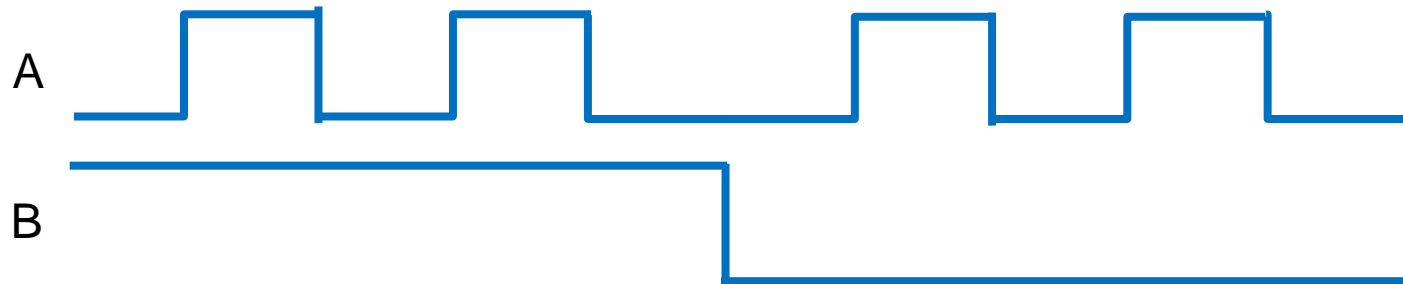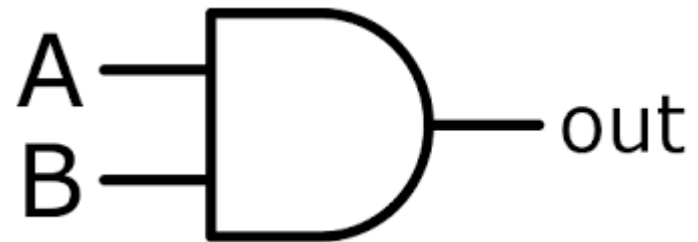
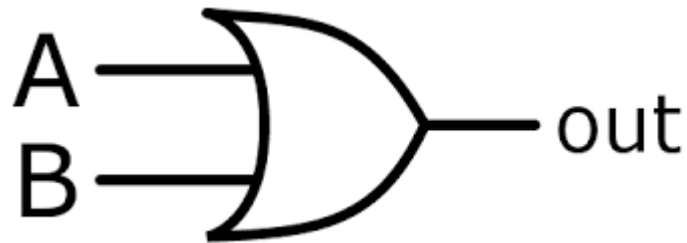
Problems

- ∞ Given that the following two-input gates are used, complete the timing diagram to show the output from both gates based on the input levels shown



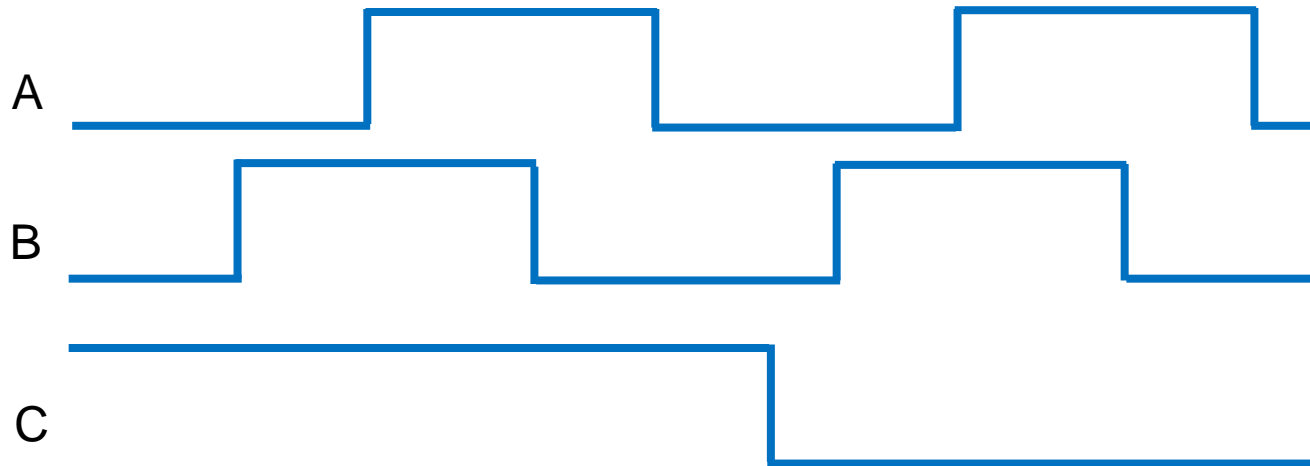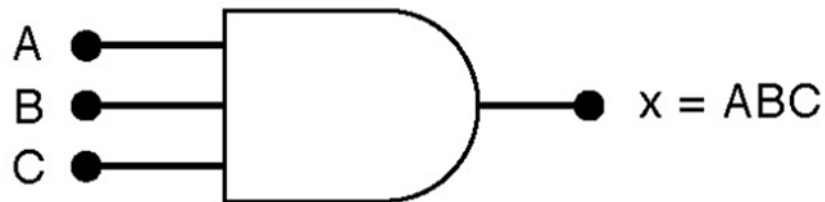
Problems

- ∞ Given that the following three-input gate is used, complete the timing diagram to show the output x from the gate based on the input levels shown



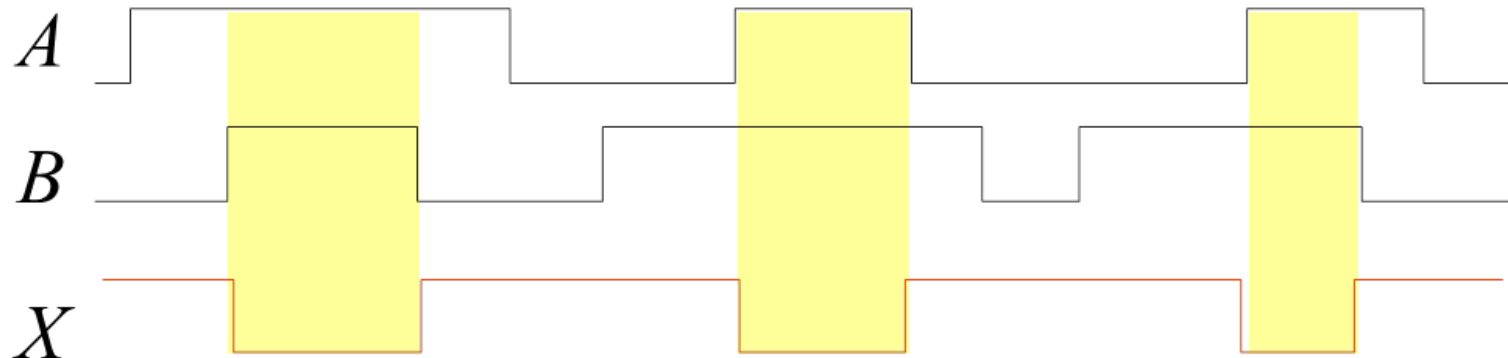Problems

- ∞ A 2-input gate produces the following timing diagram where X represents the output. What type of gate is being used?



Summary

∞ Logic gates covered today

Inverter	A logic circuit that inverts or complements its inputs.
AND gate	A logic gate that produces a HIGH output only when all of its inputs are HIGH
OR gate	A logic gate that produces a HIGH output when one or more inputs are HIGH
NAND gate	A logic gate that produces a LOW output only when all of its inputs are HIGH
NOR gate	A logic gate that produces a LOW output when one or more inputs are HIGH
Exclusive-OR gate	A logic gate that produces a HIGH output only when its two inputs are at opposite levels
Exclusive-NOR gate	A logic gate that produces a LOW output only when its two inputs are at opposite levels